

ENEL353 Computer Hardware Engineering I

Digital Logic Design Project

October 18, 2010

Group 1:

Forrest McKerchar (frm25), Henry Jenkins (hvj10), Joel Koh (jmk35), Sasha Wang (xhw11), Tracy Jackson (tnj14), Wim Looman (wgl18)

Preface

In the general the group worked in pairs while working on the project. With the use of Subversion the code was shared among the group. The numbers in Table 1 below have been calculated via the use of Subversion's blame command and personal opinions. The full Subversion log can be found on gforge¹.

Section	Authors	Coding Contribution (%)	Writing Contribution (%)
CPU	Henry Jenkins	50	16.6
	Joel Koh	40	16.6
MMU	Wim Looman	98 + 10(from CPU)	16.6
	Forrest McKerchar	2	16.6
I/O	Sasha Wang	50	16.6
	Tracy Jackson	50	16.6

Table 1: Group Contributions

¹See <http://gforge.elec.canterbury.ac.nz>

Abstract

This project aims to use VHDL to develop a digital logic design of a micro-controller. The design consists of three main components: CPU, MMU and I/O. The project was done by a team of six people - the team was divided evenly into three sub-groups, with each sub-group working mainly on one of the three components. The project's design process consisted of several steps: becoming familiar with the design problem, this included reading background information and references; choosing design decisions according to the specifications, writing the VHDL code, and testing. This report contains a detailed description of this process, in addition to technically describing the design and operation of the CPU, MMU and I/O subsystems, and also the buses that are responsible for communication between the components.

Table of Contents

[Introduction](#)

[Architectural design](#)

[Buses](#)

[Instruction Bus](#)

[Data Bus](#)

[Central Processing Unit \(CPU\)](#)

[Control Unit](#)

[Arithmetic Logic Unit \(ALU\)](#)

[Registers](#)

[Testing](#)

[Memory Management Unit \(MMU\)](#)

[Design](#)

[Control Unit](#)

[Testing](#)

[Instruction bus](#)

[Data bus](#)

[Input and Output I/O](#)

[Switch Control](#)

[Debouncer](#)

[Switch Register](#)

[Led Control](#)

[Testing](#)

[External Tools](#)

[Development Tools](#)

[Discussion](#)

[What we learnt](#)

[Conclusion](#)

[References](#)

[Appendices](#)

[Figures](#)

Introduction

Modern computer systems consist of hardware system and software system. The hardware system consists of microprocessor system and peripheral components. This project focuses on developing the microprocessor system of the computer hardware system which includes a central processing unit (CPU), memory management unit (MMU), input/output (I/O) unit and the bus.

In this project, a CPU, MMU and I/O were designed using VHDL to simulate a computer hardware system. Each unit is connected to number of buses, allowing inter-module communication. Each unit is the final result is intended for implementation on a field-programmable grid array (FPGA). An overview of the structure of the design is shown in the Figure 1.

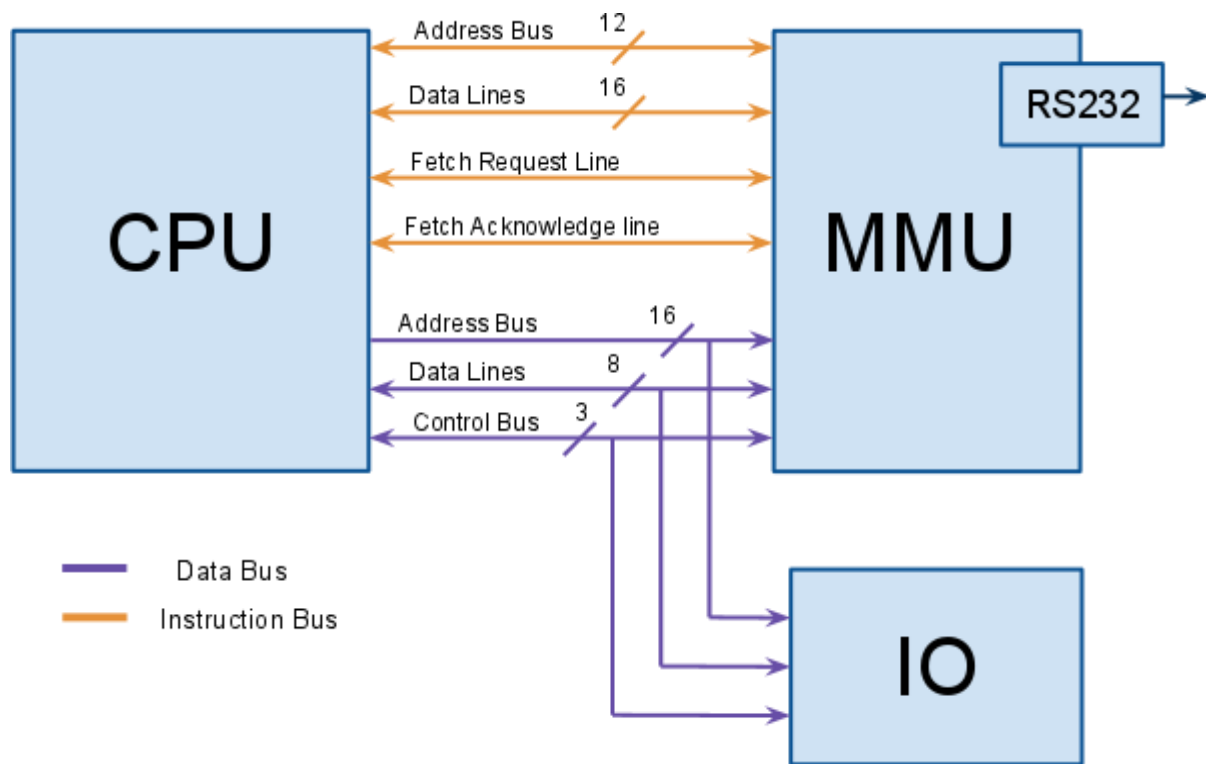


Figure 1: Overall system datapath

Architectural design

Buses

Instruction Bus

The instruction bus bi-directionally connects the CPU and the MMU carrying a 12 bit address bus, 16 bit data bus, one bit fetch request and a one bit fetch acknowledge. The fetch request is pulled low to request data and is pulled high to acknowledge the data, while the fetch acknowledge is pulled low when the data is loaded and high whenever the fetch request line goes low.

Data Bus

The data bus is connected from the CPU to both the MMU and the I/O, it carries a 16 bit address bus, 8 data lines and a 3 bit control bus. Both the data lines and the control bus are bi-directional, while the address bus is uni-directional from the CPU to either the MMU or the I/O, which is distinguished by the least significant bit.

The address bus indicates the destination of the data that the CPU is sending out. An address which has its least significant bit as a zero, indicates the data is going to the I/O, else it is a one indicating the data is going to the MMU. Therefore the I/O and MMU components both have half of the total 2¹⁶ (16 bit) addresses available.

The 3-bit control bus carries three separate lines; the read!/write (R!/W) line, the bus request line and the bus acknowledge line. When idle, the bus request line is pulled high and the bus acknowledge line is set to high impedance. Before using the data lines, the CPU pulls the bus request low and sets the R!/W line to the corresponding mode, zero for write and one for read. The bus acknowledgement line is pulled low when the MMU or the I/O has completed reading from or writing to the data lines. After which the CPU clears the bus request line and the MMU or I/O return the bus acknowledgement line to high impedance again. All the control bus changes for interaction between the CPU and MMU or I/O for reading can be seen in Table 2, and for writing can be seen in Table 3.

	R!/W	Request	Acknowledge
IDLE CPU clears R!/W and sets address then sets request	X	1	1
CHECK ADDRESS If correct address, continue, else return to IDLE	1	0	1
WRITE DATA	1	0	1

MMU/IO writes the data then set acknowledge			
WAIT CLEAR CPU clears request MMU/IO waits for request to clear then clears acknowledge	1	0	0

Table 2: Changes on control bus when CPU is reading, X implies 'do not care'

	R!/W	Request	Acknowledge
IDLE CPU clears R!/W and sets address and data then sets request	X	1	1
CHECK ADDRESS If correct address, continue, else return to IDLE	0	0	1
WRITE DATA MMU/IO reads the data then set acknowledge	0	0	1
WAIT CLEAR CPU clears request MMU/IO waits for request to clear then clears acknowledge	0	0	0

Table 3: Changes on control buss when CPU is writing, X implies 'do not care'

Central Processing Unit (CPU)

The CPU fetches an instruction from memory, decodes it, setting all the control lines, then executes the instruction. To make both the coding and the design of the CPU the whole design was broken down into several entities. As shown in Fig. 2, the main data path is from the GPR, through the ALU then back to the AL via the common data bus. Depending on the different instruction the ALU is configured to perform a different operation. The Control unit takes care of setting all the control lines. These control lines are determined by the current instruction and the values in the status register. Because the CPU is constructed out of several smaller entities, the file `cpu.vhd` is there to make sure each component is instantiated in the hardware. The `cpu.vhd` file has no logic in it, just port maps to connect all the signals.

Control Unit

The control unit controls all the data flow within the CPU by setting the control lines shown in Fig. 3. The control unit runs in a fetch, decode and execute cycle. In the fetch stage, the control unit obtains an instruction from memory in the MMU, pointed to by the program counter, in the form of an opcode. The program counter is then incremented to get ready for the next cycle.

The decode stage is when most of the data processing occurs. Depending on the opcode, the control unit will control the multiplexers and demultiplexers to select the different registers required to be written to and read from. The control unit will process the necessary data from appropriate registers or from memory. Arithmetic and logical functions, however, are passed on to the ALU to calculate, after the control lines have been set. Instructions that require registers or memory to be written to will only be marked for writing in the decode stage.

In the execute stage, registers marked for writing will be enabled, and data to be written to memory will be transferred. The registers are only enabled for writing for one clock cycle to prevent loops in the data path from constantly overriding the registers.

The control unit also supports a reset signal that resets the program counter and status register when low, corresponding to power off.

 


Figure 2: Data flow within CPU

 


Figure 3: CPU with control lines only

Arithmetic Logic Unit (ALU)

The ALU is a completely asynchronous logic entity that takes two 8 bit vectors, a four bit control line and the carry bit. The four control lines set which function is to be applied to the two 8 bit vectors. The ALU makes use of an 8 bit full adder to calculate all the required outputs. This full adder is composed of an 8 bit ripple adder. Only the ALU functions write to the status register so the input to the status register is driven directly by the ALU.

Registers

The three sets of registers, the general purpose registers, address registers and program counter/status register are all built using conditional statements that only updates the contents on the clocks rising edge. The address register also has the ability to update only 8 bits at a time as required by the specifications. All the registers are synchronous with the exception of the reset. The reset is active low so when the power is turning on the registers are reset. The reset is also able to be used to reset the program counter back to the zero address. This would allow an external reset pin or button to hard reset the whole microprocessor to be reset without having to reprogram the FPGA.

Testing

Testing of the CPU components was carried out using test benches. For each of the components a test bench file was created. These files were designed and built to test as many of the extreme cases as possible. In most of the cases, the test benches would define the inputs, wait for the clock to cycle, set some other control lines then expect an output from the module. This method worked well and brought out many bugs in our code.

Using test benches also made checking the logic easy. For most of the entities one member of the team would program the actual entity how they thought it should work, then the other team member would write the test bench. This if there was a misunderstanding of the logic, we could check it after the test bench had failed.

Memory Management Unit (MMU)

The MMU is responsible for managing all the CPU's requests for access to the instruction and data memory. The actual memory in this design is stored on a personal computer, connected to the FPGA board via an RS232 serial link. This configuration requires the MMU to interface to the RS232 link, in addition to the internal buses. Low-level interfacing to the serial link is achieved via the use of a supplied minimal UART core, originally obtained from OpenCores.org.

Design

The MMU essentially consists of bus mux/demuxers, which are controlled by a control unit. The control unit is formed from a number of finite state machines

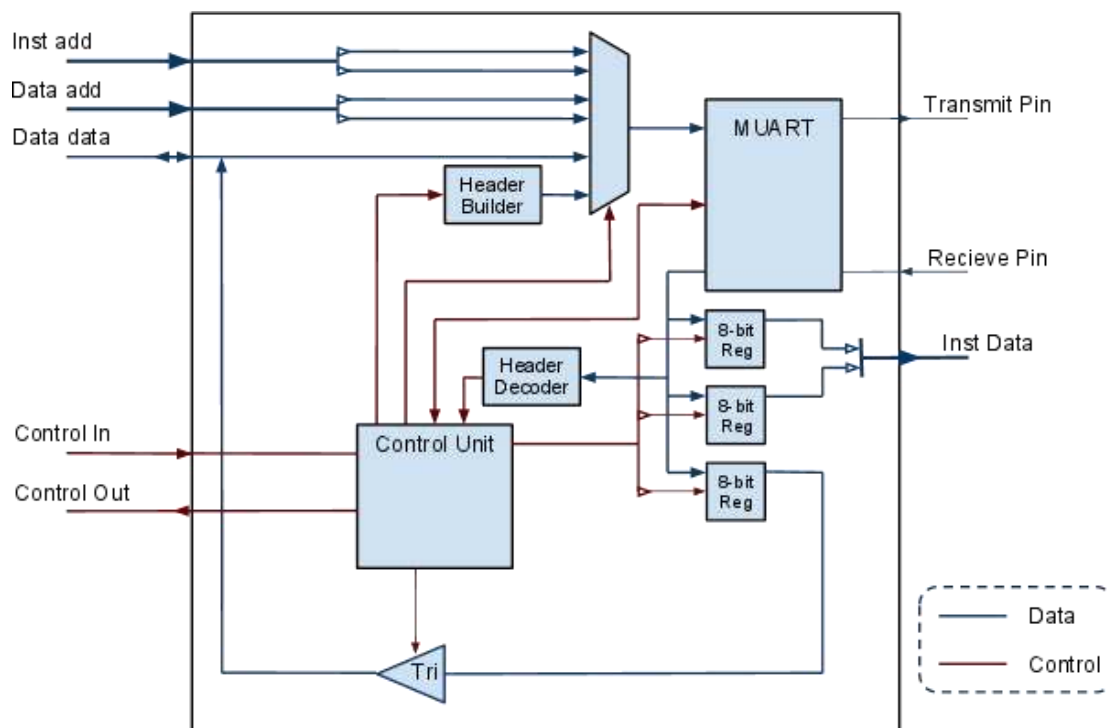


Figure 4: Data and Control paths of the MMU.

Control Unit

The control unit was split into two separate parts, the instruction control unit and the data control unit. This was mainly done to reduce the control unit file size and logic, but did mean there was some duplication of code. Each of these control units consists of 4 separate Finite State Machines (FSM), arranged in a simple hierarchy:

 


Figure 5: MMU Control Unit state machines

The lower level FSMs are activated during specific states of the higher level FSMs - the higher levels wait for the lower levels to reach their finished state, then move on to their own next state.

The highest level FSM (see Figures 10 and 11), `state`, is required to determine when the bus is activated, and to start the `get_state` FSM. Once the `get_state` FSM returns, then the `state` FSM will set the correct ack signal to low, to inform the CPU that the data is available. After this, it waits till the CPU withdraws its data request, and then sets the ack signal back to its idle state.

The `get_state` FSM (see Figures 12 and 13) simply encodes the order of sending and fetching data bytes. For the instruction control unit this is a simple linear state machine, while for the data control unit it has one choice, based off whether it is receiving or transmitting the data.

In the individual states of the `get_state` FSM, the `read` and `transmit` FSMs (see Figures 14 and 15) are activated, so that they receive or transmit the specific data currently in need of processing.

Testing

There were two test benches developed to test the MMU. One tested purely the instruction bus, whilst the other tested the data bus in conjunction with the IO unit.

- Instruction bus

The test bench developed to test the instruction bus (found in `mmu/mmu_tb.vhd`) creates and links the MMU to an extra MUART, which simulates the computer providing the memory. The address bus and request line are driven by the test bench and the data being transferred between the MMU and the MUART is then analysed and compared to what ideally should be being transferred. One full memory request, and part of a subsequent one, can be seen below: the test bench sets the `inst_add` bus, then pulls `inst_req` low. This initiates the memory transfer and causes first the header, then the low byte of the address and finally the high byte of the address to be written to the MUART, this can be seen below in Figure 6. The fake computer then responds with a header, address bytes and data bytes, and the output of the MMU is compared to the expected data.

 


Figure 6: Instruction bus testing waveforms

- Data bus

The data bus test bench was almost identical. Its only difference was that it instantiated a copy of the IO unit as well, and had updated code to handle communication with the IO. When this was run with the IO unit deactivated it worked, however there were bus contention issues with the data bus when both the MMU and IO units were active.

Input and Output I/O

The I/O component is responsible for displaying the CPU's output and takes user requests for the CPU. The design of the I/O component uses 2 push buttons and 8 LEDs and consists of 5 entities: I/O, led, switch, switch register and switch debounce. The connection of these entities can be seen in Figure 7, where the I/O component is only connected to the CPU not the MMU.

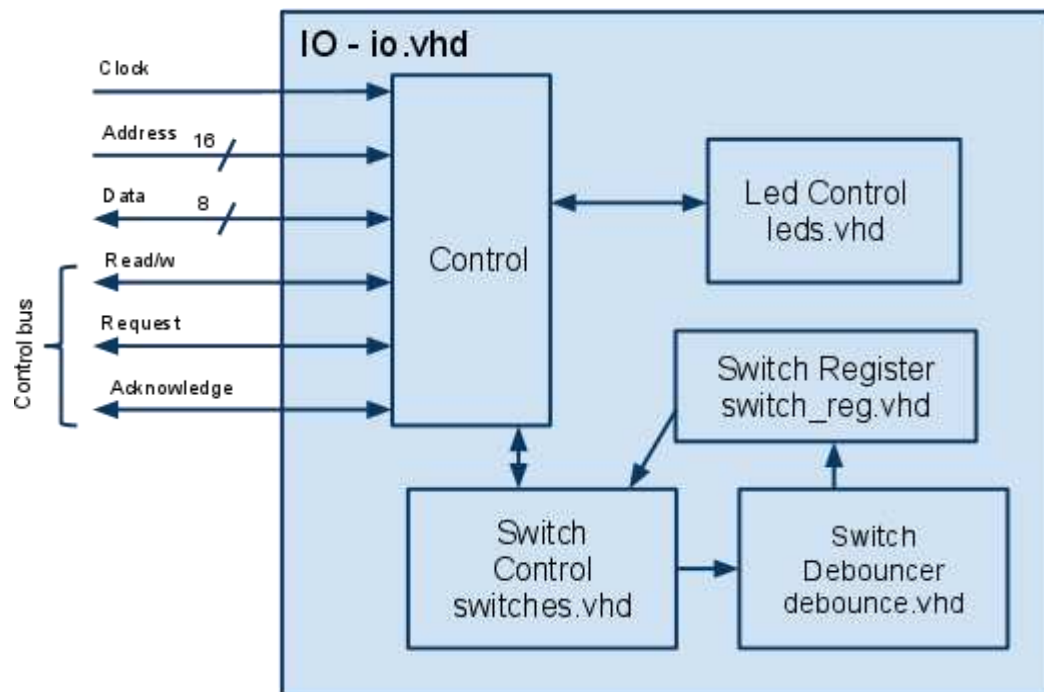


Figure 7: An overview of the I/O component's structure

Switch Control

When an input push button is pressed, a logic high is generated on the associated FPGA pin. This signal first goes through the debouncer and then is passed to the CPU on request.

Debouncer

A push button debouncer is implemented in the switch control design. When a push button is pressed, the signal does not change from one voltage to another cleanly[1], Figure 8. The signal varies up and down before settling to its final voltage. The problem can result in the system receiving multiple button presses when only a single button press is given.

 


Figure 8 - Button depress “bouncing” waveform

The switch debouncer that is implemented in this design distinguishes a single button press from multiple button presses. It takes the button input and only once it has been continuously high for eight clock cycles does it output that the button is pressed.

Switch Register

A switch register is a register that stores a button press before the CPU collects this information. It is placed immediately after the switch debouncer. The “enable” port is set to low once the output of the register is high which means the register will not accept any more input when a button press is stored in the switch register. The “enable” port of the switch register is set back to high when the acknowledge bit is set to low which means the button press information is loaded on the data bus to the CPU and the switch register is ready to take new input.

Switch registers are needed because not all button presses are sent to the CPU immediately, it needs to be stored until the CPU asks for it. The current design of the switch register can only store one button press.

When the CPU asks the information about button presses (i.e. the R/!W is 1, the data request is 0 and the address is one of the buttons), the switch register will load the information onto the data bus. Then the acknowledge bit of the control bus will be set to low by the I/O component.

Figure 9 shows a simple illustration of the current implementation for one switch. The address bus and R/!W, request signal is omitted in the diagram.

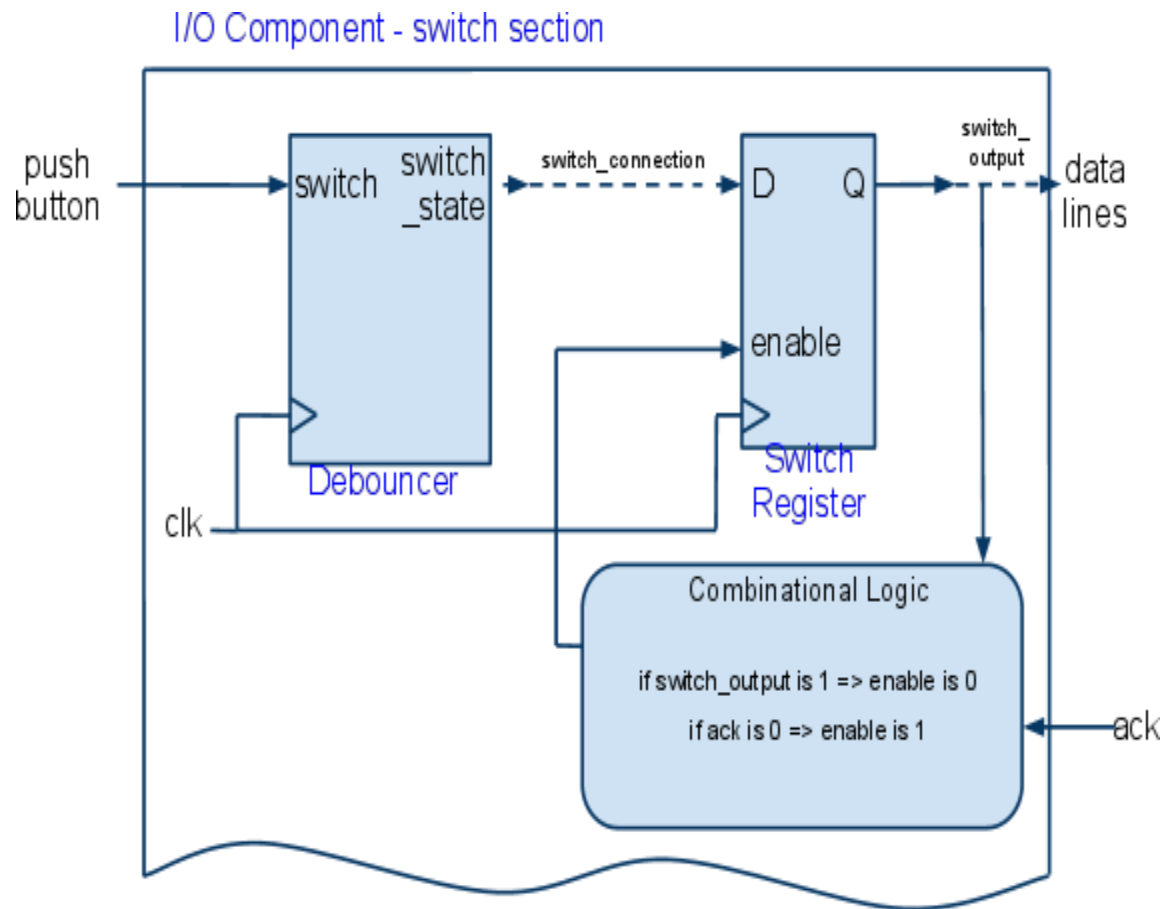


Figure 9: Switch Control

Led Control

All 8 output LEDs are accessed through the same address, in this case each bit of the 8 bit data line represents the on/off state of one LED, e.g. if the data on the data line is '11000011' then the first two and last two leds would be turned on and the other leds would be stayed off. When the CPU sets the address bus to that of the LEDs, the data line gets stored in an 8 bit register and outputted to the LEDs, the acknowledge bit of the control bus is pulled low until the CPU has reset the request bit of the control bus back to high.

Testing

Testing was carried out by implementing the code in Xilinx as a new project. In the test project a button is debounced and sets the data bus to turn the LEDs on.

Tools

Developed

Assembler

A two-pass assembler was developed in Ruby. The first pass scans the file for labels and records their absolute position within the file. The second pass then scans each line and breaks it up into opcode and operands, depending on the instruction in the line different functions are called to convert the operands into their bit pattern representation. The opcode and operands determined are then combined and added to the current output.

This was tested using a simple input file and comparing the output by hand to the expected values.

Memory Provider

A memory provider was also developed in Ruby utilising the `ruby-serialport` gem² for access to the computers serial port. This takes in a program file generated from the assembler and optionally an initial data file, a possible extension to the assembler would be to have it generate this data file from constants in the assembly file. These input files are then stored in arrays and accessed according to the MMUs instruction over the serial line.

This was not tested for two reasons, a lack of time and no access to installing the `ruby-serialport` gem on the computers at Uni. While the MMU was fully working in the end there was not enough time to develop a simple test that for example could connect to the memory provider and just display the data in specific addresses. Also while the computers at Uni had Ruby installed, they lacked the Ruby Gem management program and attempts at compiling it failed so the gem required for the low level hardware access could not be installed.

Utilised

While developing the VHDL code several tools were used. Xilinx ISE was used to check the syntax and schematics, Subversion for code management and then GHDL was used to run the test benches.

As we did not have access to Modelsim, the best method we came up with to run test benches was to use GHDL. GHDL is an open source simulator. This allowed the test benches to assert the outputs from entities and write to stdout if something unexpected happens. GHDL was also able to generate signal waveforms that could be opened in GTKWave and verified.

²<http://ruby-serialport.rubyforge.org/>

Discussion

Currently the design units have not been successfully integrated into a single system due to time constraints.

I/O

Future Implementation

The switch register can easily be modified to process concurrent button presses. The control section also needs to be implemented to interface with and handle the data bus, this would allow for easier expansion of the system in terms of I/O devices.

This would, for example, allow a particular button to be used for ending the input. The CPU would then be able to perform different tasks for 1 button press, 2 button presses or different button combinations.

CPU

Because of the modular design of the CPU, implementing pipe lining would be simple. As the code is modular, all the original code could be reused, allowing the pipeline entities to interface between the existing CPU entities. The only original code that would need to be changed would be the `cpu.vhd` file. The port maps would also need to be rearranged to include any new code.

Because of time constraints, the CPU as a whole was not able to be simulated and tested. Tests such as those written for the ALU and registers were purely localised, setting an input and expecting an output. The control unit however, was a much larger entity that required data to flow to and from the ALU, various registers as well as memory from the MMU. This made it a lot harder to write test benches for its testing and simulation. However, this could have been implemented had more time been provided.

MMU

Queueing was not implemented in the MMU. In order to provide queueing functionality, cache registers and extra control logic would need to be developed. The bus would need to have extra functionality also, allowing the MMU to request data to be sent to the CPU, after it has been read successfully from the serial link.

Communications between group members

The group initially met to discuss the project. During this meeting, the respective design modules were assigned to groups of two group members. During the course of the project, the sub-groups met together to develop their individual modules, while all-inclusive top-level group meetings still occasionally took place. Towards the end of the design stage, meetings involving all group members increased in frequency, as the modules were integrated into the top-level design.

During the report preparation, the whole team actively collaborated together using the Google Documents online application. This meant each team member could actively take part in discussing what everyone

else was working on. This vastly improved the productivity of the team over conventional methods - the report was written more accurately and efficiently.

Problems with the design

When the group is trying to combine all the part together, it is realised that the I/O component should connect to the MMU rather than directly to the CPU. However the functionality of the I/O is the same except all the buses come out of the I/O should directed to the MMU.

What we learnt

We learnt that unforeseen issues can often arise, so adequate time needs to be allocated to allow for testing and fixing problems and bugs.

We have learnt how to code circuits using VHDL and how to implement these as a digital circuit on a FPGA through Xilinx. As well as how small errors in the VHDL code can implement a completely different digital circuit, for example latches.

Latches were also an issue during stages of the development. We learnt to change latches into flip-flops by synchronising them with the clock signal, by placing the code inside process blocks, which are sensitive to the clock signal.

We also learnt how to use test benches to verify the circuits we were implementing followed the specifications. This was just using GHDL but the same test benches with slight tweaks should be valid in ModelSim or ISim, the Xilinx ISE simulator.

Conclusion

In conclusion, the majority of each separate unit has been completed, but not successfully integrated due to time constraints. The code for the whole design has been well thought out, with the design developed to work. With the right tools and more time, the solution could be completed. Overall, the group worked well as a whole and as pairs. Separating the project into three sections meant that the pairs could get together regularly to team code, especially while trying to learn the syntax of VHDL. The end results of the project were that all group members now have a greater understanding of hardware design techniques, and how to implement them in the VHDL language.

References

- [1] A. Greensted, The Lab Book Pages, June 2010, [Online], Available: <http://www.labbookpages.co.uk/electronics/debounce.html>
- [2] Brown, Stephen D. , Vranesic, Zvonko G; Fundamentals of digital logic with VHDL design; 3rd ed; McGraw-Hill, 2009.
- [3] D. A. Patterson, J. L. Hennessy, “The Processor: Datapath and Control,” in Computer Organization and Design, 3th ed.Elsevier, 2005, ch. 5.
- [4] P. P. Chu, FPGA prototyping by VHDL examples: Xilinx Spartan-3 version.Wiley-Interscience, 2008.
- [5] P.P. Chu, RTL hardware design using VHDL coding for efficiency, portability and scalability, Wiley-Interscience, 2006.
- [6] T. Gingold, GHDL guide, 2007, [Online], Available: <http://ghdl.free.fr/ghdl/>

Appendices

Appendix A: Figures

 


Figure 10: Main data control unit state machine.

 


Figure 11: Main instruction control unit state machine.

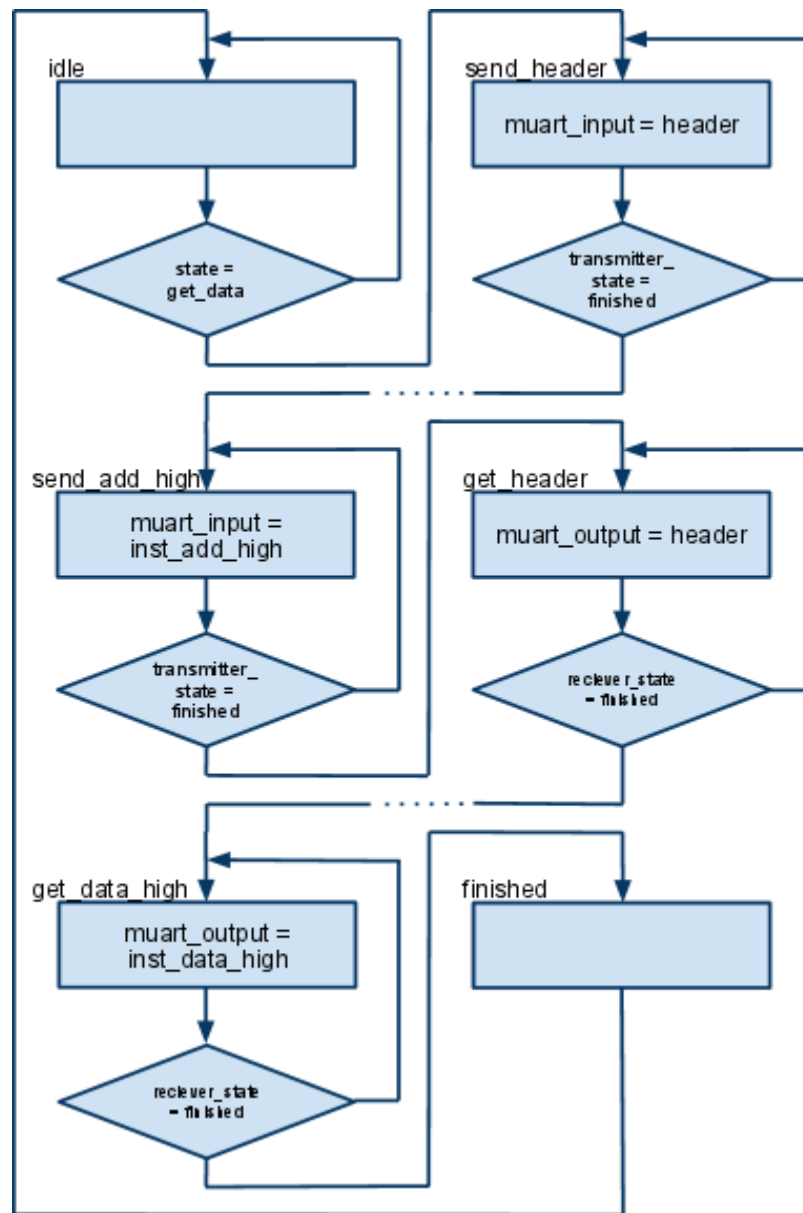


Figure 12: Instruction control unit transferring states.

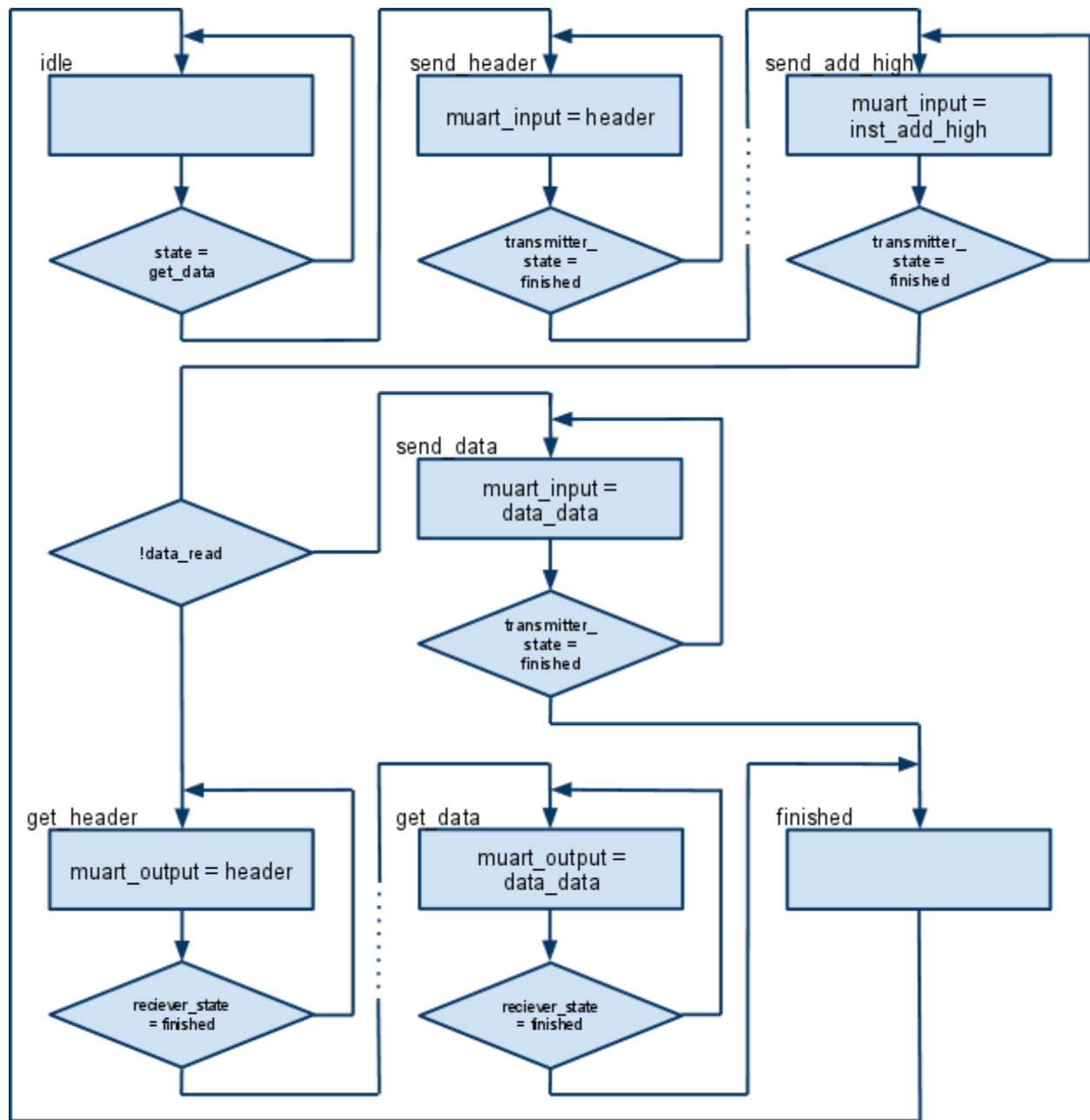


Figure 13: Data control unit transferring states.

 


Figure 14: Receive state machine.

 


Figure 15: Transmit state machine.

Appendix B: Code listing

Listings

Main

Listing 1: main.vhd

```
1  -- Authors:
   --      Wim Looman, Forrest McKerchar, Henry Jenkins, Joel Koh, Sasha Wang, Tracy
       Jackson
3
4  library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
6
7  library work;
8
9  entity main is
10     port (
11         clk      : in  std_logic;
12         reset    : in  std_logic;
13         tx       : out std_logic;
14         rx       : in  std_logic;
15         sw1      : in  std_logic;
16         sw2      : in  std_logic;
17     );
18     end main;
19
20     architecture main_arch of main is
21         component cpu IS
22             PORT(
23                 -- instruction bus
24                 inst_add  : out std_logic_vector(11 downto 0); -- Address lines.
25                 inst_data : in  std_logic_vector(15 downto 0); -- Data lines.
26                 inst_req  : out std_logic;                      -- Pulled low to request bus
27                                     usage.
28                 inst_ack  : in  std_logic;                      -- Pulled high to inform of
29                                     request completion.
30                 -- data bus
31                 data_add  : out std_logic_vector(15 downto 0); -- Address lines.
32                 data_line : inout std_logic_vector(7 downto 0); -- Data lines.
33                 data_read : out std_logic;                      -- High for a read request,
34                                     low for a write request.
35                 data_req  : out std_logic;                      -- Pulled low to request bus
36                                     usage.
37                 data_ack  : inout std_logic;                    -- Pulled high to inform of
38                                     request completion.
39                 -- extras
40                 clk       : in  std_logic;
41                 reset     : in  std_logic;
42             );
43         end component;
44         component mmu_main is
45             port (
46                 -- instruction bus
47                 inst_add  : in  std_logic_vector(11 downto 0); -- Address lines.
48                 inst_data : out std_logic_vector(15 downto 0); -- Data lines.
49                 inst_req  : in  std_logic;                      -- Pulled low to request bus
50                                     usage.
51                 inst_ack  : out std_logic;                      -- Pulled high to inform of
52                                     request completion.
53             );
54         end component;
55     end architecture;
```

```

47     -- data bus
data_add  : in    std_logic_vector(15 downto 0); -- Address lines.
data_line : inout std_logic_vector(7  downto 0); -- Data lines.
49     data_read : in    std_logic;                -- High for a read request,
        low for a write request.
data_req  : in    std_logic;                -- Pulled low to request bus
        usage.
51     data_ack  : inout std_logic;                -- Pulled high to inform of
        request completion.
        -- extras
53     clk       : in    std_logic;
receive_pin : in    std_logic;
55     transfer_pin : out std_logic
    );
57 END component;
component IO is
59     PORT(
        -- data bus --
61     data_add  : IN    std_logic_vector(15 DOWNT0 0); -- address lines --
data_data  : INOUT std_logic_vector(7  DOWNT0 0); -- data lines --
63     data_read : INOUT std_logic;                -- pulled high for
        read, low for write --
data_req  : INOUT std_logic;                -- pulled low to
        request bus usage --
65     data_ack  : INOUT std_logic;                -- pulled high to
        inform request completion --
        -- io --
67     clk       : IN    std_logic;
sw1       : IN    std_logic;
69     sw2       : IN    std_logic);
        --leds      : OUT std_logic_vector(7 DOWNT0 0);
71 END component;
-- instruction bus
73 signal inst_add  : std_logic_vector(11 downto 0); -- Address lines.
signal inst_data : std_logic_vector(15 downto 0); -- Data lines.
75 signal inst_req  : std_logic;                -- Pulled low to request bus
        usage.
signal inst_ack  : std_logic;                -- Pulled high to inform of
        request completion.
77 -- data bus
signal data_add  : std_logic_vector(15 downto 0); -- Address lines.
79 signal data_line : std_logic_vector(7  downto 0); -- Data lines.
signal data_read : std_logic;                -- High for a read request, low
        for a write request.
81 signal data_req  : std_logic;                -- Pulled low to request bus
        usage.
signal data_ack  : std_logic;                -- Pulled high to inform of
        request completion.
83
begin
85     c : cpu port map(
        -- instruction bus
87     inst_add => inst_add, -- Instruction address
inst_data => inst_data, -- Instruction data
89     inst_req => inst_req, -- Request
inst_ack => inst_ack, -- Instruction obtained
91     -- data bus
data_add => data_add, -- Data address
93     data_line => data_line, -- Data
data_read => data_read, -- 1 for read, 0 for write
95     data_req => data_req, -- Request
data_ack => data_ack, -- Data written to/ read from
97     -- extras
clk      => clk,
99     reset  => reset
    );
101    m : mmu_main port map(
        -- instruction bus
103    inst_add  => inst_add, -- Address lines.
inst_data  => inst_data, -- Data lines.
105    inst_req  => inst_req, -- Pulled low to request bus usage.
inst_ack  => inst_ack, -- Pulled high to inform of request completion.
107    -- data bus

```

```

109     data_add      => data_add,  -- Address lines.
    data_line      => data_line, -- Data lines.
    data_read      => data_read, -- High for a read request, low for a write request.
111    data_req       => data_req,  -- Pulled low to request bus usage.
    data_ack       => data_ack,  -- Pulled high to inform of request completion.
113    -- extras
    clk            => clk,
115    receive_pin    => rx,
    transfer_pin   => tx
117 );
i : io  port map(
119     clk            => clk,
    data_add        => data_add,
121     data_data      => data_line,
    data_read       => data_read,
123     data_req       => data_req,
    data_ack        => data_ack,
125     -- io --
    sw1             => sw1,
127     sw2            => sw2
);
129 end architecture main_arch;

```

IO

Listing 2: IO/debounce.vhd

```
1  -----
2  -- Module Name:      debounce
3  -- Description: Entity to debounce a mechanical switch/button
4  -- Authors: Tracy Jackson
5  --               Sasha Wang
6  --
7  -----
8
9  library IEEE;
10 use IEEE.STD_LOGIC_1164.ALL;
11 use IEEE.STD_LOGIC_ARITH.ALL;
12 use IEEE.STD_LOGIC_UNSIGNED."+";
13
14 library work;
15
16 ENTITY debounce IS
17     PORT(clk : IN STD_LOGIC;
18           switch : IN STD_LOGIC;
19           switch_state : OUT STD_LOGIC);
20 END debounce;
21
22 ARCHITECTURE debounced_switch OF debounce IS
23     SIGNAL count : STD_LOGIC_VECTOR(2 DOWNTO 0);
24 BEGIN
25     -- Debounce the switch using a counter
26     PROCESS(clk, switch)
27     BEGIN
28         IF switch = '0' THEN
29             count <= "000";
30         ELSIF rising_edge(clk) THEN
31             IF count /= "111" THEN
32                 count <= count + 1;
33             END IF;
34         END IF;
35         IF count = "111" AND switch = '1' THEN
36             switch_state <= '1';
37         ELSE
38             switch_state <= '0';
39         END IF;
40     END PROCESS;
41 END debounced_switch;
```

Listing 3: IO/IO.vhd

```
1  -----
2  -- Module Name:      IO
3  -- Description: Entity to handle IO
4  -- Authors: Tracy Jackson
5  --               Sasha Wang
6  --
7  -----
8
9  library IEEE;
10 use IEEE.STD_LOGIC_1164.ALL;
11 use IEEE.STD_LOGIC_ARITH.ALL;
12 --use IEEE.STD_LOGIC_UNSIGNED.ALL;
13
14 library work;
15 use work.debounce;
16 use work.switch_reg;
17 use work.led_io;
18
19
20 ---- Uncomment the following library declaration if instantiating
21 ---- any Xilinx primitives in this code.
22 --library UNISIM;
23 --use UNISIM.VComponents.all;
```

```

24 entity IO is
25     PORT(
26         -- data bus --
27         data_add      : IN          std_logic_vector(15 DOWNTO 0);
28         -- address lines --
29         data_data      : INOUT       std_logic_vector(7 DOWNTO 0);  -- data
30         lines --
31         data_read      : INOUT       std_logic;
32         -- pulled high for read, low for write --
33         data_req        : INOUT      std_logic;
34         -- pulled low to request bus usage --
35         data_ack        : INOUT      std_logic;
36         -- pulled high to inform request completion --
37         -- io --
38         clk            : IN          std_logic;
39         sw1            : IN          std_logic;
40         sw2            : IN          std_logic);
41         --leds          : OUT std_logic_vector(7 DOWNTO 0);
42 end IO;
43
44 architecture io of IO is
45
46     COMPONENT led_io
47     PORT(
48         data_add      : IN          std_logic_vector(15 DOWNTO 0);  --
49         address lines --
50         data_data      : INOUT       std_logic_vector(7 DOWNTO 0);  -- data lines
51         --
52         data_read      : INOUT       std_logic;                      --
53         pulled high for read, low for write --
54         data_req        : INOUT      std_logic;                      --
55         pulled low to request bus usage --
56         data_ack        : INOUT      std_logic;                      --
57         pulled high to inform request completion --
58         clock          : IN          std_logic
59     );
60     END COMPONENT;
61
62     COMPONENT switch_io IS
63     PORT ( data_add      : IN          std_logic_vector(15 DOWNTO 0);
64           data_data      : INOUT       std_logic_vector(7 DOWNTO 0);
65           data_read      : INOUT       std_logic;
66           data_req        : INOUT      std_logic;
67           data_ack        : INOUT      std_logic;
68           clk            : IN          std_logic;
69           sw1            : IN          std_logic;
70           sw2            : IN          std_logic
71     );
72     END COMPONENT;
73
74 BEGIN
75     led: led_io PORT MAP(data_add, data_data, data_read, data_req, data_ack, clk);
76     switch: switch_io PORT MAP(data_add, data_data, data_read, data_req, data_ack,
77                               clk,sw1,sw2);
78
79     -----
80 END io;

```

Listing 4: IO/leds.vhd

```

-----
2 -- Module Name:      led_io
3 -- Description: Entity control output LEDs
4 -- Authors: Tracy Jackson
5 --                Sasha Wang

```

```

6  --
  -----
8  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
10 use IEEE.STD_LOGIC_ARITH.ALL;

12 library work;

14 ENTITY led_io IS
   PORT(
16         data_add      : IN          std_logic_vector(15 DOWNTO 0);
           -- address lines --
         data_data      : INOUT       std_logic_vector(7 DOWNTO 0);  -- data
           lines --
18         data_read     : INOUT       std_logic;
           -- pulled high for read, low for write --
         data_req       : INOUT       std_logic;
           -- pulled low to request bus usage --
20         data_ack      : INOUT       std_logic;
           -- pulled high to inform request completion --
           --
22         clock         : IN          std_logic;
           );
24 END led_io;

26 ARCHITECTURE led_arch OF led_io IS
   Signal led_enable    : std_logic;
28   Signal led_state     : std_logic_vector(7 DOWNTO 0);
   BEGIN
30
   -- Determine if it is the LEDs being accessed
32   PROCESS(clock, data_req, data_add, data_read)
   BEGIN
34       IF data_req = '0' AND data_add = "0000000000001110" AND data_read = '0'
           THEN
36               led_enable <= '1';
           ELSE
38               led_enable <= '0';
           END IF;
40   END PROCESS;

   -- process of data from the CPU and output to LEDs
42   PROCESS(clock, led_enable)
   BEGIN
44       IF rising_edge(clock) THEN
           IF led_enable = '1' THEN
46               led_state <= data_data;
               data_ack <= '0';
48           END IF;
           END IF;
50   END PROCESS;

52

54 END led_arch;

```

Listing 5: IO/switch_register.vhd

```

1  -----
   -- Module Name:      switch_reg
3  -- Description: Entity to store switch state (can be extended to more than one)
   -- Authors: Tracy Jackson
5  --               Sasha Wang
   --
7  -----
   library IEEE;
9  use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.STD_LOGIC_ARITH.ALL;
11 use IEEE.STD_LOGIC_UNSIGNED.ALL;

13 library work;

```

```

15 ENTITY switch_reg IS
    PORT( D          : IN STD_LOGIC;
17         clk,enable : IN STD_LOGIC;
           Q          : OUT STD_LOGIC);
19 END switch_reg;

21 ARCHITECTURE reg_arch OF switch_reg IS
    BEGIN
23         PROCESS(D, enable, clk)
            BEGIN
25             IF rising_edge(clk) THEN --Need else there???
                    IF enable = '1' THEN
27                 Q <= D;
                    END IF;
29             END IF;
            END PROCESS;
31 END reg_arch;

```

Listing 6: IO/switches.vhd

```

1  -----
  -- Module Name:      switch_io
3  -- Description: Entity to control input from switches
  -- Authors: Tracy Jackson
  --               Sasha Wang
  --
7  -----
    library IEEE;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.STD_LOGIC_ARITH.ALL;

11   library work;
13   use work.debounce;
15   use work.switch_reg;

    entity switch_io is
17       PORT(
19           -- data bus --
           data_add      : IN          std_logic_vector(15 DOWNT0 0);
           -- address lines --
           data_data      : INOUT      std_logic_vector(7 DOWNT0 0);  -- data
           lines --
21           data_read     : INOUT      std_logic;
           -- pulled high for read, low for write --
           data_req       : INOUT      std_logic;
           -- pulled low to request bus usage --
23           data_ack      : INOUT      std_logic;
           -- pulled high to inform request completion --
           -- io --
25           clk           : IN          std_logic;
           sw1            : IN          std_logic;
27           sw2            : IN          std_logic);
    end switch_io;

29   architecture Behavioral of switch_io is
31
33   signal enable1          : std_logic;
35   signal switch1_connection : std_logic;
37   signal enable2          : std_logic;
39   signal switch2_connection : std_logic;
41   signal switch2_output    : std_logic;

43   COMPONENT debounce
       PORT(clk, switch : IN STD_LOGIC;
            switch_state: OUT STD_LOGIC);
45   END COMPONENT;

47   COMPONENT switch_reg

```

```

        PORT( D           : IN STD_LOGIC;
49          clk, enable : IN STD_LOGIC;
              Q           : OUT STD_LOGIC);
51 END COMPONENT;

53

55 BEGIN

57 sw1_debouncer: debounce PORT MAP(clk, sw1, switch1_connection);
  sw1_status: switch_reg PORT MAP(switch1_connection,clk, enable1, switch1_output);
59

61 sw2_debouncer: debounce PORT MAP(clk, sw2,switch2_connection);
  sw2_status: switch_reg PORT MAP(switch2_connection,clk, enable2, switch2_output);
63

65 PROCESS(clk,switch1_output,switch2_output, data_ack)
  BEGIN
67 IF rising_edge(clk) THEN
    IF switch1_output = '1' AND data_ack = 'Z' THEN --when the switch_reg has stored
      1, disable switch_reg from getting any more info
69     enable1 <= '0';

71     --ELSIF data_ack = '0' AND data_add = "0000000000001110" THEN -- when the data is
      sent to the CPU, enable the switch_reg again
    -- enable1 <= '1';
73 ELSE
    enable1 <= '1';
75 END IF;

77 IF switch2_output = '1' AND data_ack = 'Z' THEN --when the switch_reg has stored
      1, disable switch_reg from getting any more info
    enable2 <= '0';
79

    --ELSIF data_ack = '0' AND data_add = "0000000000001100" THEN -- when the data is
      sent to the CPU, enable the switch_reg again
81    -- enable2 <= '1';
    ELSE
83      enable2 <= '1';
    END IF;
85

87 END IF;
  END PROCESS;
89

91 PROCESS(clk, data_add, data_read)
  BEGIN
93 IF rising_edge(clk) THEN
    IF data_req = '0' AND data_read = '1' THEN
95      IF data_add = "0000000000001110" THEN -- switch1 address
        IF switch1_output = '1' THEN
97          data_data <= "00000001";
        ELSE
99          data_data <= "00000000";
        END IF;
101      data_ack <= '0';
    END IF;
103    IF data_add = "0000000000001100" THEN -- switch2 address
      IF switch2_output = '1' THEN
105        data_data <= "00000001";
      ELSE
107        data_data <= "00000000";
      END IF;
109      data_ack <= '0';
    END IF;
111    ELSIF data_req = '1' AND data_ack = '0' THEN
      data_ack <= 'Z';
113    END IF;
  END IF;
115 END PROCESS;

```


117

119

END Behavioral;

CPU

Listing 7: processor/alu.vhd

```
-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
6 use IEEE.NUMERIC_STD.ALL;
use ieee.std_logic_arith.all;
8 --use ieee.std_logic_unsigned.all;

10
library work;
12 use work.fulladder8;
--use work.cpu.ALL;
14
-- Uncomment the following library declaration if using
16 -- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
18
-- Uncomment the following library declaration if instantiating
20 -- any Xilinx primitives in this code.
--library UNISIM;
22 --use UNISIM.VComponents.all;

24 entity alu is
    Port (f      : in    STD_LOGIC_VECTOR (3 downto 0); -- Function (opcode)
26         rx     : in    STD_LOGIC_VECTOR (7 downto 0); -- Input x (Rx)
         ry     : in    STD_LOGIC_VECTOR (7 downto 0); -- Input y (Ry)
28         ro     : out   STD_LOGIC_VECTOR (7 downto 0); -- Output Normaly (Ry)
         Cin    : in    STD_LOGIC;                    -- Carry in
30         sr     : out   STD_LOGIC_VECTOR (15 downto 0)); -- Status register out Z(0),
                C(1), N(2)
    end alu;
32

34 architecture alu_arch of alu is
    component fulladder8 IS
36     Port (A      : in    STD_LOGIC_VECTOR( 7 downto 0);
         B      : in    STD_LOGIC_VECTOR( 7 downto 0);
38         Cin    : in    STD_LOGIC;
         Sum    : out   STD_LOGIC_VECTOR( 7 downto 0);
40         Cout   : out   STD_LOGIC
        );
42    end component;
    signal A      : std_logic_vector(7 downto 0);
44    signal B      : std_logic_vector(7 downto 0);
    signal AdderCin : std_logic;
46    signal Sum    : std_logic_vector(7 downto 0);
    signal AdderCout : std_logic;
48    signal Z,C,N  : std_logic; -- Make the code easier to read
    signal output  : std_logic_vector(7 downto 0); -- used to allow reading of ro
50 BEGIN
    Adder: fulladder8 port map(A, B, AdderCin, Sum, AdderCout);
52    process(f, rx, ry, Cin, Sum, AdderCout)
        --signal Z,C,N : std_logic; -- Make the code easier to read
54    BEGIN
        -- use case statement to achieve
56        -- different operations of ALU

58        AdderCin <= '0';
        A <= (others => '0');
60        B <= (others => '0');
        output <= (others => '0');
62        C <= '0';
        N <= '0';
64        IF f = "0001" THEN -- Do AND operation
            output <= ry and rx;
66        ELSIF f = "0011" THEN -- Do OR operation
            output <= ry or rx;
```

```

68     ELSIF f = "0101" THEN
        output <= not rx;
70     ELSIF f = "0111" THEN -- Do XOR operation
        output <= ry xor rx;
72     ELSIF f = "1001" THEN -- Do ADD operation
        AdderCin <= '0';
74         A <= ry;
        B <= rx;
76         output <= Sum;
        ELSIF f = "1011" THEN -- Do ADC operation
78         AdderCin <= Cin;
        A <= ry;
80         B <= rx;
        output <= Sum;
82     ELSIF f = "1101" THEN -- Do SUB operation
        AdderCin <= '1';
84         A <= ry;
        B <= (not rx);
86         output <= Sum;
        ELSIF f = "1111" THEN -- Do SBB operation
88         AdderCin <= (not Cin);
        A <= ry;
90         B <= (not rx);
        output <= Sum;
92     ELSIF f = "0100" THEN -- Do NEG operation ( two's complement )
        AdderCin <= '1';
94         A <= (others => '0');
        B <= (not rx);
96         output <= Sum;
        C <= AdderCout;
98         N <= output(7);
        ELSIF f = "0110" THEN -- Do CMP operation
100         AdderCin <= '1';
        A <= rx;
102         B <= (not ry);
        output <= Sum;
104         C <= AdderCout;
        N <= output(7);
106     ELSE
        AdderCin <= '0';
108         A <= (others => '0');
        B <= (others => '0');
110         output <= (others => '0');
        C <= '0';
112         N <= '0';
        END IF;
114 --     if (output = "00000000") then -- Set the Zero in status register
--         sr(0) <= '1';
116 --     ELSE
--         sr(0) <= '0';
118 --     end if;

120     C <= AdderCout; -- Carry is always 0
    N <= output(7); -- This might need to be changed to '0'
122     ro <= output;
end process;
124     Z <= not (output(0) AND output(1) AND output(2) AND output(3) AND output(4)
        AND output(5) AND output(6) AND output(7));
126     sr(0) <= Z; --Z(0)
    sr(1) <= C; --C(1)
128     sr(2) <= N; --N(2)
    sr(15 downto 3) <= (others => '0');
130
end alu_arch;

```

Listing 8: processor/ar.vhd

```

1 -- Authors:
--     Henry Jenkins, Joel Koh
3
library IEEE;
5 use IEEE.STD_LOGIC_1164.ALL;

```

```

7  library work;
   use work.reg16;
9
   entity ar is
11  Port (clk           : in    STD_LOGIC;
        enable         : in    STD_LOGIC;
13        Sel8Bit       : in    STD_LOGIC;
        SelHighByte    : in    STD_LOGIC;
15        ByteInput     : in    STD_LOGIC_VECTOR (7 downto 0);
        SelRi          : in    STD_LOGIC_VECTOR (1 downto 0);    -- Select the address
                                register
17        SelRo         : in    STD_LOGIC_VECTOR (1 downto 0);    -- Select the address
                                register
        Ri             : in    STD_LOGIC_VECTOR (15 downto 0);    -- The input
19        Ro            : out   STD_LOGIC_VECTOR (15 downto 0));    -- The output
   end ar;
21
   architecture Behavioral of ar is
23     component reg16 IS
        port(I          : in    std_logic_vector(15 downto 0);
25              clock    : in    std_logic;
              enable    : in    std_logic;
27              reset    : in    std_logic;
              Q          : out   std_logic_vector(15 downto 0)
29            );
     end component;
31
     signal ROE      : std_logic; -- Enable signals
33     signal R1E      : std_logic;
     signal R2E      : std_logic;
35     signal input    : std_logic_VECTOR (15 downto 0);
     signal Q0        : std_logic_VECTOR (15 downto 0);
37     signal Q1        : std_logic_VECTOR (15 downto 0);
     signal Q2        : std_logic_VECTOR (15 downto 0);
39 BEGIN
     reg_0 : reg16 port map(input, clk, ROE, '0', Q0);
41     reg_1 : reg16 port map(input, clk, R1E, '0', Q1);
     reg_2 : reg16 port map(input, clk, R2E, '0', Q2);
43
     SetInput: process(clk, enable, SelRi, Ri)
45     BEGIN
         ROE <= '0';
47         R1E <= '0';
         R2E <= '0';
49         IF enable = '1' THEN
             case SelRi IS
51                 WHEN "00" =>
                     ROE <= '1';
53                 WHEN "01" =>
                     R1E <= '1';
55                 WHEN "10" =>
                     R2E <= '1';
57                 WHEN others =>
                     NULL; -- None of them are enabled
59             END CASE;
         END IF;
61     end process;

63     -- Select if 1 or 2 Bytes is to be written and if
     SetNumBytes: process(clk, Ri, SelRi, ByteInput, Sel8Bit, SelHighByte, Q0, Q1, Q2)
65     BEGIN
         IF Sel8Bit = '0' THEN
67             input <= Ri;
         ELSE
69             if SelHighByte = '1' THEN
                 input(15 downto 8) <= ByteInput;
71                 case SelRi IS
                     WHEN "00" =>
73                     input(7 downto 0) <= Q0(7 downto 0);
                     WHEN "01" =>
75                     input(7 downto 0) <= Q1(7 downto 0);
                     WHEN others =>

```

```

77         input(7 downto 0) <= Q2(7 downto 0);
       END CASE;
79     else
       input(7 downto 0) <= ByteInput;
81     case SelRi IS
       WHEN "00" =>
83         input(15 downto 8) <= Q0(15 downto 8);
       WHEN "01" =>
85         input(15 downto 8) <= Q1(15 downto 8);
       WHEN others =>
87         input(15 downto 8) <= Q2(15 downto 8);
       END CASE;
89     END IF;
    END IF;
91 end process;

93 -- Set the output Ro
    WITH SelRo SELECT
95     Ro <= Q0 WHEN "00",
        Q1 WHEN "01",
97         Q2 WHEN others;
    end Behavioral;

```

Listing 9: processor/cpu.vhd

```

1  -- Authors:
   --      Henry Jenkins, Joel Koh
3
   library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
   --use IEEE.STD_LOGIC_ARITH.ALL;
7  --use IEEE.STD_LOGIC_UNSIGNED.ALL;

9  library work;
   use work.alu;
11  use work.cu;
   use work.ar;
13  use work.gpr;
   use work.sr;
15  use work.pc;

17
   ---- Uncomment the following library declaration if instantiating
19   ---- any Xilinx primitives in this code.
   --library UNISIM;
21  --use UNISIM.VComponents.all;

23  entity cpu is
25      PORT(
       -- instruction bus
27         inst_add  : out std_logic_vector(11 downto 0); -- Address lines.
         inst_data  : in  std_logic_vector(15 downto 0); -- Data lines.
29         inst_req   : out std_logic;                    -- Pulled low to request bus
           usage.
         inst_ack   : in  std_logic;                    -- Pulled high to inform of
           request completion.
31         -- data bus
         data_add   : out std_logic_vector(15 downto 0); -- Address lines.
33         data_line  : inout std_logic_vector(7 downto 0); -- Data lines.
         data_read  : out std_logic;                    -- High for a read request,
           low for a write request.
35         data_req   : out std_logic;                    -- Pulled low to request bus
           usage.
         data_ack   : inout std_logic;                  -- Pulled high to inform of
           request completion.
37         -- extras
         clk        : in  std_logic;
39         reset     : in  std_logic
       );
41 end cpu;

```

```

43 architecture cpu_arch of cpu is
44     component alu IS
45         Port (f      : in  STD_LOGIC_VECTOR (3 downto 0);  -- Function (opcode)
46              rx      : in  STD_LOGIC_VECTOR (7 downto 0);  -- Input x (Rx)
47              ry      : in  STD_LOGIC_VECTOR (7 downto 0);  -- Input y (Ry)
48              ro      : out STD_LOGIC_VECTOR (7 downto 0);  -- Output Normally (Ry)
49              Cin      : in  STD_LOGIC;                    -- Carry in
50              sr      : out STD_LOGIC_VECTOR (15 downto 0)); -- Status register out Z(0),
51                      C(1), N(2)
52     END component;
53     component ar is
54         Port (clk      : in  STD_LOGIC;
55              enable    : in  STD_LOGIC;
56              Sel8Bit   : in  STD_LOGIC;
57              SelHighByte : in  STD_LOGIC;
58              ByteInput : in  STD_LOGIC_VECTOR (7 downto 0);
59              SelRi      : in  STD_LOGIC_VECTOR (1 downto 0);  -- Select the address
60                      register
61              SelRo      : in  STD_LOGIC_VECTOR (1 downto 0);  -- Select the address
62                      register
63              Ri         : in  STD_LOGIC_VECTOR (15 downto 0);  -- The input
64              Ro         : out STD_LOGIC_VECTOR (15 downto 0)); -- The output
65     END component;
66     component cu IS
67         Port (reset      : in  STD_LOGIC;                    -- '0' for reset
68              clock       : in  STD_LOGIC;                    -- clock
69
70              alu_f       : out STD_LOGIC_VECTOR (3 downto 0); -- Function
71              alu_Cin      : out STD_LOGIC;                    -- Carry in to ALU
72
73              -- General Purpose Registers
74              gpr_InSel    : out STD_LOGIC;                    -- select the input path (0
75                      - cu, 1 - ALU)
76              gpr_en       : out STD_LOGIC;                    -- enable write to GPR
77              gpr_SelRx    : out STD_LOGIC_VECTOR (2 downto 0); -- select GPR output x
78              gpr_SelRy    : out STD_LOGIC_VECTOR (2 downto 0); -- select GPR output y
79              gpr_SelRi    : out STD_LOGIC_VECTOR (2 downto 0); -- select GPR input
80              gpr_Ri       : out STD_LOGIC_VECTOR (7 downto 0); -- input to GPR
81              gpr_Rx       : in  STD_LOGIC_VECTOR (7 downto 0); -- output Rx from GPR
82              --gpr_Ry     : in  STD_LOGIC_VECTOR (7 downto 0); -- output Ry from GPR ,
83                      not used
84
85              -- Status Register
86              sr_en        : out STD_LOGIC;                    -- enable write to SR
87              sr_reset     : out STD_LOGIC;                    -- reset SR
88              sr_Ro        : in  STD_LOGIC_VECTOR (15 downto 0); -- output from SR
89              -- control unit doesnt write to SR, the ALU does
90
91              -- Program Counter
92              pc_en        : out STD_LOGIC;                    -- enable write to PC
93              pc_reset     : out STD_LOGIC;                    -- reset PC
94              pc_Ri        : out STD_LOGIC_VECTOR (15 downto 0); -- input to PC
95              pc_Ro        : in  STD_LOGIC_VECTOR (15 downto 0); -- output from PC
96
97              -- Address Registers
98              ar_en        : out STD_LOGIC;                    -- enable write to AR
99              ar_SelRi     : out STD_LOGIC_VECTOR (1 downto 0); -- select AR in
100             ar_SelRo     : out STD_LOGIC_VECTOR (1 downto 0); -- select AR out
101             ar_Ri        : out STD_LOGIC_VECTOR (15 downto 0); -- input to AR
102             ar_Ro        : in  STD_LOGIC_VECTOR (15 downto 0); -- output from AR
103             ar_sel8Bit   : out STD_LOGIC;                    -- only write half the AR
104             ar_selHByte  : out STD_LOGIC;                    -- high or low half of the
105                     AR to write
106             ar_ByteIn    : out STD_LOGIC_VECTOR (7 downto 0); -- 8 bit input to write
107                     half of AR
108
109             -- Instruction memory
110             inst_add     : out STD_LOGIC_VECTOR (11 downto 0); -- Instruction address
111             inst_data    : in  STD_LOGIC_VECTOR (15 downto 0); -- Instruction data
112             inst_req     : out STD_LOGIC;                    -- Request
113             inst_ack     : in  STD_LOGIC;                    -- Instruction obtained

```

```

109      data_add      : out STD_LOGIC_VECTOR (15 downto 0); -- Data address
      data_data      : inout STD_LOGIC_VECTOR (7 downto 0); -- Data
111      data_read     : out STD_LOGIC;                      -- 1 for read, 0 for write
      data_req       : out STD_LOGIC;                      -- Request
113      data_ack      : in STD_LOGIC                       -- Data written to/ read
          from

115  );
  END component;
117  component gpr is
  Port (clk          : in  STD_LOGIC;
119        enable      : in  STD_LOGIC;
        SelRx        : in  STD_LOGIC_VECTOR (2 downto 0); -- The Rx output selection
          value
121        SelRy       : in  STD_LOGIC_VECTOR (2 downto 0); -- The Ry output selection
          value
        SelRi        : in  STD_LOGIC_VECTOR (2 downto 0); -- The Ri input selection
          value
123        SelIn       : in  STD_LOGIC; -- Select where the input should be from the CU
          or CDB
        RiCU         : in  STD_LOGIC_VECTOR (7 downto 0); -- Input from the Control
          Unit
125        RiCDB       : in  STD_LOGIC_VECTOR (7 downto 0); -- Input from the Common
          Data Bus
        Rx           : out STD_LOGIC_VECTOR (7 downto 0); -- The Rx output
127        Ry          : out STD_LOGIC_VECTOR (7 downto 0); -- The Ry output
  END component;
129  component sr is
  Port (clk          : in  STD_LOGIC;
131        enable      : in  STD_LOGIC;
        reset        : in  STD_LOGIC;
133        Ri          : in  STD_LOGIC_VECTOR (15 downto 0); -- The input to the SR
        Ro           : out STD_LOGIC_VECTOR (15 downto 0)); -- The output from SR
135  END component;
  component pc is
137  Port (clk          : in  STD_LOGIC;
        enable      : in  STD_LOGIC;
139        reset        : in  STD_LOGIC;
        Ri          : in  STD_LOGIC_VECTOR (15 downto 0); -- The input to the SR
141        Ro           : out STD_LOGIC_VECTOR (15 downto 0); -- The output from SR
  END component;
143  signal alu_Cin      : std_logic;
  signal alu_f         : std_logic_vector(3 downto 0);
145  signal alu_rx       : std_logic_vector(7 downto 0);
  signal alu_ry        : std_logic_vector(7 downto 0);
147
  signal sr_reset      : std_logic;
149  signal sr_enable     : std_logic;
  signal sr_Ro         : std_logic_vector(15 downto 0);
151  signal sr_input      : std_logic_vector(15 downto 0);

153  signal ar_enable     : STD_LOGIC; -- enable write to AR
  signal ar_SelRi       : STD_LOGIC_VECTOR (1 downto 0); -- select AR in
155  signal ar_SelRo      : STD_LOGIC_VECTOR (1 downto 0); -- select AR out
  signal ar_Ri          : STD_LOGIC_VECTOR (15 downto 0); -- input to AR
157  signal ar_Ro         : STD_LOGIC_VECTOR (15 downto 0); -- output from AR
  signal ar_sel8Bit     : STD_LOGIC; -- only write half the AR
159  signal ar_selHByte   : STD_LOGIC; -- high or low half of the AR
      to write
  signal ar_ByteIn      : STD_LOGIC_VECTOR (7 downto 0); -- 8 bit input to write half
      of AR

161
  signal pc_reset      : std_logic;
163  signal pc_enable     : std_logic;
  signal pc_Ri         : std_logic_vector(15 downto 0);
165  signal pc_Ro         : std_logic_vector(15 downto 0);

167  signal gpr_InSel    : std_logic;
  signal gpr_enable    : std_logic;
169  signal gpr_SelRx     : std_logic_vector(2 downto 0);
  signal gpr_SelRy     : std_logic_vector(2 downto 0);
171  signal gpr_SelRi     : std_logic_vector(2 downto 0);
  signal gpr_RiCU      : std_logic_vector(7 downto 0);

```

```

173 signal gpr_RiCDB : std_logic_vector(7 downto 0);
begin
175
176     a: alu port map(
177         f      => alu_f,
178         rx     => alu_rx,
179         ry     => alu_ry,
180         ro     => gpr_RiCDB,
181         Cin    => alu_Cin,
182         sr     => sr_input
183     );
184     c: cu port map(
185
186         reset    => reset, -- '0' for reset
187         clock    => clk,  -- clock
188
189         alu_f    => alu_f, -- Function
190         alu_Cin  => alu_Cin, -- Carry into the ALU
191
192         -- General Purpose Registers
193         gpr_InSel => gpr_InSel, -- select the input path (0 - cu, 1 - ALU)
194         gpr_en    => gpr_enable, -- enable write to GPR
195         gpr_SelRx => gpr_SelRx, -- select GPR output x
196         gpr_SelRy => gpr_SelRy, -- select GPR output y
197         gpr_SelRi => gpr_SelRi, -- select GPR input
198         gpr_Ri    => gpr_RiCU, -- input to GPR
199         gpr_Rx    => alu_rx, -- Rx from GPR
200         --gpr_Ry   => alu_ry, -- Ry from GPR
201
202         -- Status Register
203         sr_en     => sr_enable, -- enable write to SR
204         sr_reset  => sr_reset, -- reset SR
205         sr_Ro     => sr_Ro, -- output from SR
206         -- control unit doesnt write to SR, the ALU does
207
208         -- Program Counter
209         pc_en     => pc_enable, -- enable write to PC
210         pc_reset  => pc_reset, -- reset PC
211         pc_Ri     => pc_Ri, -- input to PC
212         pc_Ro     => pc_Ro, -- output from PC
213
214         -- Address Registers
215         ar_en     => ar_enable, -- enable write to AR
216         ar_SelRi  => ar_SelRi, -- select AR in
217         ar_SelRo  => ar_SelRo, -- select AR out
218         ar_sel8Bit => ar_sel8Bit,
219         ar_selHByte => ar_selHByte,
220         ar_ByteIn => ar_ByteIn,
221         ar_Ri     => ar_Ri, -- input to AR
222         ar_Ro     => ar_Ro, -- output from AR
223
224         -- Instruction memory
225         inst_add  => inst_add, -- Instruction address
226         inst_data => inst_data, -- Instruction data
227         inst_req  => inst_req, -- Request
228         inst_ack  => inst_ack, -- Instruction obtained
229
230         data_add  => data_add, -- Data address
231         data_data => data_line, -- Data
232         data_read => data_read, -- 1 for read, 0 for write
233         data_req  => data_req, -- Request
234         data_ack  => data_ack, -- Data written to/ read from
235     );
236     address : ar port map(
237         clk      => clk,
238         enable   => ar_enable,
239         sel8Bit  => ar_sel8Bit,
240         selHighByte => ar_selHByte,
241         ByteInput => ar_ByteIn,
242         selRi    => ar_SelRi,
243         selRo    => ar_SelRo,
244         Ri       => ar_Ri,
245         Ro       => ar_Ro

```



```

    );
247 g : gpr port map(
        clk      => clk,
249         enable => gpr_enable,
        SelRx    => gpr_SelRx,
251         SelRy  => gpr_SelRy,
        SelRi    => gpr_SelRi,
253         SelIn  => gpr_InSel,
        RiCU     => gpr_RiCU,
255         RiCDB  => gpr_RiCDB,
        Rx       => alu_rx,
257         Ry     => alu_ry
    );
259 s : sr port map(
        clk      => clk,
261         enable => sr_enable,
        reset    => sr_reset,
263         Ri     => sr_input,
        Ro       => sr_Ro
265     );
    programcounter: pc port map(
267         clk      => clk,
        enable    => pc_enable,
269         reset    => pc_reset,
        Ri        => pc_Ri,
271         Ro       => pc_Ro
    );
273 end cpu_arch;

```

Listing 10: processor/cu.vhd

```

1  -- Authors:
   --      Henry Jenkins, Joel Koh
3
   library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.NUMERIC_STD.ALL;
7  use ieee.std_logic_arith.all;
   --use ieee.std_logic_unsigned.all;
9
11 library work;
   --use work.fulladder;
13 --use work.cpu.ALL;
15 -- Uncomment the following library declaration if using
   -- arithmetic functions with Signed or Unsigned values
17 --use IEEE.NUMERIC_STD.ALL;
19 -- Uncomment the following library declaration if instantiating
   -- any Xilinx primitives in this code.
21 --library UNISIM;
   --use UNISIM.VComponents.all;
23
   entity cu is
25     Port (reset      : in STD_LOGIC;           -- '0' for reset
           clock       : in STD_LOGIC;           -- clock
27
           alu_f       : out STD_LOGIC_VECTOR (3 downto 0); -- Function
29     alu_Cin        : out STD_LOGIC;           -- Carry in to ALU
31
           -- General Purpose Registers
           gpr_InSel   : out STD_LOGIC;           -- select the input path (0
               -- cu, 1 - ALU)
33     gpr_en         : out STD_LOGIC;           -- enable write to GPR
           gpr_SelRx   : out STD_LOGIC_VECTOR (2 downto 0); -- select GPR output x
35     gpr_SelRy     : out STD_LOGIC_VECTOR (2 downto 0); -- select GPR output y
           gpr_SelRi   : out STD_LOGIC_VECTOR (2 downto 0); -- select GPR input
37     gpr_Ri        : out STD_LOGIC_VECTOR (7 downto 0); -- input to GPR
           gpr_Rx      : in STD_LOGIC_VECTOR (7 downto 0); -- output Rx from GPR
39     --gpr_Ry      : in STD_LOGIC_VECTOR (7 downto 0); -- output Ry from GPR ,
           not used

```

```

41      -- Status Register
      sr_en      : out STD_LOGIC;           -- enable write to SR
43      sr_reset   : out STD_LOGIC;           -- reset SR
      sr_Ro      : in STD_LOGIC_VECTOR (15 downto 0); -- output from SR
45      -- control unit doesnt write to SR, the ALU does

47      -- Program Counter
      pc_en      : out STD_LOGIC;           -- enable write to PC
49      pc_reset   : out STD_LOGIC;           -- reset PC
      pc_Ri      : out STD_LOGIC_VECTOR (15 downto 0); -- input to PC
51      pc_Ro      : in STD_LOGIC_VECTOR (15 downto 0); -- output from PC

53      -- Address Registers
      ar_en      : out STD_LOGIC;           -- enable write to AR
55      ar_SelRi   : out STD_LOGIC_VECTOR (1 downto 0); -- select AR in
      ar_SelRo   : out STD_LOGIC_VECTOR (1 downto 0); -- select AR out
57      ar_Ri      : out STD_LOGIC_VECTOR (15 downto 0); -- input to AR
      ar_Ro      : in STD_LOGIC_VECTOR (15 downto 0); -- output from AR
59      ar_sel8Bit : out STD_LOGIC;           -- only write half the AR
      ar_selHByte : out STD_LOGIC;           -- high or low half of the
      AR to write
61      ar_ByteIn  : out STD_LOGIC_VECTOR (7 downto 0); -- 8 bit input to write
      half of AR

63      -- Instruction memory
      inst_add    : out STD_LOGIC_VECTOR (11 downto 0); -- Instruction address
65      inst_data  : in STD_LOGIC_VECTOR (15 downto 0); -- Instruction data
      inst_req    : out STD_LOGIC;           -- Request
67      inst_ack   : in STD_LOGIC;           -- Instruction obtained

69      data_add   : out STD_LOGIC_VECTOR (15 downto 0); -- Data address
      data_data   : inout STD_LOGIC_VECTOR (7 downto 0); -- Data
71      data_read  : out STD_LOGIC;           -- 1 for read, 0 for write
      data_req    : out STD_LOGIC;           -- Request
73      data_ack   : in STD_LOGIC;           -- Data written to/ read
      from

75  );
end cu;
77

79 architecture Behavioral of cu is
    component fulladder16 IS
81  Port (A      : in  STD_LOGIC_VECTOR(15 downto 0);
        B      : in  STD_LOGIC_VECTOR(15 downto 0);
83  Cin  : in  STD_LOGIC;
        Sum   : out  STD_LOGIC_VECTOR(15 downto 0);
85  Cout : out  STD_LOGIC
        );
87  end component;

89  type states is (reset_state, fetch, decode, execute);
  signal state      : states := reset_state;
91  signal next_state : states := reset_state;

93  signal opcode     : std_logic_vector(15 downto 0); -- unprocessed instruction

95  -- Decoded data
  signal rx : std_logic_vector(2 downto 0);
97  signal ry : std_logic_vector(2 downto 0);
  signal ay : std_logic_vector(1 downto 0);
99
  -- Indicates what needs to be executed
101 signal write_gpr    : std_logic;
  signal write_sr      : std_logic;
103 signal write_pc     : std_logic;
  signal write_ar      : std_logic;
105 signal write_memory : std_logic;

107 -- full adders
  signal A16      : std_logic_vector(15 downto 0);
109 signal B16      : std_logic_vector(15 downto 0);

```

```

111 signal    AdderCin16    : std_logic;
signal    Sum16           : std_logic_vector(15 downto 0);
signal    AdderCout16    : std_logic;

113
115 signal v      : STD_LOGIC_VECTOR(7 downto 0);  -- 8-bit immediate

117 BEGIN
    Adder16: fulladder16 port map(A16, B16, AdderCin16, Sum16, AdderCout16);

119
    -- Process instruction
    -- Assumes all instructions are valid
121 process(clock, state, opcode, gpr_Rx, sr_Ro, pc_Ro, ar_Ro, inst_data, inst_ack,
        data_data, data_ack,
123         rx, ry, ay, v, write_gpr, write_sr, write_pc, write_ar, write_memory)
    BEGIN
125         if rising_edge(clock) then
            case state is
127                 when reset_state =>
                    sr_reset <= '0';
129                     pc_reset <= '0';
                    next_state <= fetch;

131
                    when fetch =>
133                         sr_reset <= '1';
                        pc_reset <= '1';

135
                        gpr_en <= '0';
137                         sr_en <= '0';
                        pc_en <= '0';
139                         ar_en <= '0';

141
                        write_gpr <= '0';
                        write_sr <= '0';
143                         write_pc <= '0';
                        write_ar <= '0';
145                         write_memory <= '0';

147
                        inst_add <= pc_Ro(11 downto 0);
                        if inst_ack = '0' then
149                             inst_req <= '1';
                        else
151                             opcode <= inst_data;
                            inst_req <= '0';

153
                            -- increment program counter
155                             AdderCin16 <= '1';
                            A16 <= PC_Ro;
157                             B16 <= "0000000000000000";
                            pc_Ri <= Sum16;
159                             pc_en <= '1';

161
                            next_state <= decode;
                        end if;
163                     when decode =>
                            pc_en <= '0';

165
                            -- ALU
167                             if opcode(15) = '0' and opcode(10) = '0' and not opcode(14 downto 11) =
                                "0010" then

169
                                    ry <= opcode(7 downto 5);
                                    rx <= opcode(2 downto 0);

171
                                    gpr_SelRy <= ry;
                                    gpr_SelRx <= rx;
                                    gpr_SelRi <= ry;
173                                     gpr_InSel <= '1';
                                    alu_f <= opcode(14 downto 11);
175                                     alu_Cin <= sr_Ro(1);  -- Carry

177
                                    if not opcode(14 downto 11) = "0110" then -- CMP doesnt write to gpr, all
                                        others do

```

```

181         write_gpr <= '1';
    end if;

183     write_sr <= '1';
    next_state <= execute;

185
-- Branching
187     elsif opcode(11 downto 10) = "11" then

189         v <= "00000000"; -- initialise v

191         if opcode(15) = '1' then
            case opcode(14 downto 12) is
193                 when "000" => -- BEQ
                    if sr_Ro(0) = '1' then -- Z=1
195                        v <= opcode(9 downto 2);
                    end if;
197                 when "001" => -- BNE
                    if sr_Ro(0) = '0' then -- Z=0
199                        v <= opcode(9 downto 2);
                    end if;
201                 when "010" => -- BLT
                    if sr_Ro(0) = '0' and sr_Ro(2) = '1' then -- Z=0 and N=1
203                        v <= opcode(9 downto 2);
                    end if;
205                 when "011" => -- BGT
                    if sr_Ro(0) = '0' and sr_Ro(2) = '0' then -- Z=0 and N=0
207                        v <= opcode(9 downto 2);
                    end if;
209                 when "100" => -- BC
                    if sr_Ro(1) = '1' then -- C=1
211                        v <= opcode(9 downto 2);
                    end if;
213                 when "101" => -- BNC
                    if sr_Ro(1) = '0' then -- C=0
215                        v <= opcode(9 downto 2);
                    end if;
217                 when "110" => -- RJMP
                    v <= opcode(9 downto 2);

219
                    when others =>
221                        v <= "00000000";
            end case;

223
            -- PC <- PC + v
225            AdderCin16 <= '0';
            A16 <= PC_Ro;
227            B16 <= "00000000" & v;
            pc_Ri <= Sum16;

229
            elsif opcode(15 downto 12) = "0111" then -- JMP
231                ay <= opcode(6 downto 5);

233
                -- PC <- ay
                ar_SelRo <= ay;
235                pc_Ri <= ar_Ro;
            else
237                -- should not reach here
                pc_Ri <= pc_Ro; -- no change
239            end if;

241            write_pc <= '1';
            next_state <= execute;

243
-- Addressing
245     else
247         gpr_Insel <= '0';

249         case opcode(12 downto 10) is

251             when "001" => -- Load
                if opcode(15) = '1' then -- immediate

```

```

253         rx <= '0' & opcode(1 downto 0);
254         v <= opcode(9 downto 2);
255
256         -- rx <- v
257         gpr_SelRi <= rx;
258         gpr_Ri <= v;
259         write_gpr <= '1';
260         next_state <= execute;
261     else -- direct
262         rx <= opcode(2 downto 0);
263         ay <= opcode(6 downto 5);
264
265         -- rx <- [ay]
266         gpr_SelRi <= rx;
267         ar_selRo <= ay;
268         data_add <= ar_Ro;
269         data_read <= '1';
270         if data_ack = '0' then -- request data
271             data_req <= '1';
272         else -- data obtained
273             gpr_Ri <= data_data;
274             data_req <= '0';
275             write_gpr <= '1';
276
277         case opcode(14 downto 13) is
278             when "01" => -- auto increment
279                 AdderCin16 <= '1';
280                 A16 <= ar_Ro;
281                 B16 <= "0000000000000000";
282                 ar_selRi <= ay;
283                 ar_sel8bit <= '0';
284                 ar_Ri <= Sum16;
285                 write_ar <= '1';
286             when "10" => -- auto decrement
287                 AdderCin16 <= '0';
288                 A16 <= ar_Ro;
289                 B16 <= "1111111111111111";
290                 ar_selRi <= ay;
291                 ar_sel8bit <= '0';
292                 ar_Ri <= Sum16;
293                 write_ar <= '1';
294             when others =>
295                 -- do nothing
296         end case;
297         next_state <= execute;
298     end if;
299 end if;
300
301 when "101" => -- Store
302     if opcode(15) = '1' then -- immediate
303         ay <= opcode(1 downto 0);
304         v <= opcode(9 downto 2);
305
306         -- [ay] <- v
307         ar_selRo <= ay;
308         data_add <= ar_Ro;
309         data_read <= '0';
310         data_data <= v;
311         write_memory <= '1';
312         next_state <= execute;
313     else -- direct
314         rx <= opcode(2 downto 0);
315         ay <= opcode(6 downto 5);
316
317         -- [ay] <- rx
318         gpr_selRx <= rx;
319         ar_selRo <= ay;
320         data_add <= ar_Ro;
321         data_read <= '0';
322         data_data <= gpr_Rx;
323         write_memory <= '1';
324
325         case opcode(14 downto 13) is

```

```

327         when "01" => -- auto increment
            AdderCin16 <= '1';
            A16 <= ar_Ro;
329            B16 <= "0000000000000000";
            ar_selRi <= ay;
331            ar_sel8bit <= '0';
            ar_Ri <= Sum16;
333            write_ar <= '1';
            when "10" => -- auto decrement
335                AdderCin16 <= '0';
                A16 <= ar_Ro;
337                B16 <= "1111111111111111";
                ar_selRi <= ay;
339                ar_sel8bit <= '0';
                ar_Ri <= Sum16;
341                write_ar <= '1';
            when others =>
343                -- do nothing
            end case;
345            next_state <= execute;
        end if;
347
    when "100" => -- Move
349        if opcode(9) = '1' then
            rx <= opcode(2 downto 0);
351            ay <= opcode(6 downto 5);

353            -- ayn <- rx
            gpr_selRx <= rx;
355            ar_selRi <= ay;
            ar_sel8bit <= '1';
357            ar_ByteIn <= gpr_Rx;

359            if opcode(8) = '1' then -- high
                ar_selHByte <= '1';
361            else -- low
                ar_selHByte <= '0';
363            end if;

365            write_ar <= '1';
            next_state <= execute;
367
        elsif opcode(4) = '1' then
369            rx <= opcode(7 downto 5);
            ay <= opcode(1 downto 0);
371

            -- rx <- ayn
            gpr_selRi <= rx;
373            ar_selRo <= ay;
375

            if opcode(3) = '1' then -- high
377                gpr_Ri <= ar_Ro(15 downto 8);
            else -- low
379                gpr_Ri <= ar_Ro(7 downto 0);
            end if;

381            write_gpr <= '1';
            next_state <= execute;
383

        else
385            rx <= opcode(2 downto 0);
            ry <= opcode(7 downto 5);
387

389            -- ry <- rx
            gpr_SelRx <= rx;
            gpr_SelRi <= ry;
391            gpr_Ri <= gpr_Rx;
393

            write_gpr <= '1';
            next_state <= execute;
395

397        end if;

```

```

399         when others =>
401             -- should not reach here

403     end case;

405 end if;

407 when execute =>
408     if write_memory = '1' then
409         if data_ack = '0' then -- request write
410             data_req <= '1';
411         else -- data written
412             data_req <= '0';
413             gpr_en <= write_gpr;
414             sr_en <= write_sr;
415             pc_en <= write_pc;
416             ar_en <= write_ar;
417             next_state <= fetch;
418         end if;
419     else
420         gpr_en <= write_gpr;
421         sr_en <= write_sr;
422         pc_en <= write_pc;
423         ar_en <= write_ar;
424         next_state <= fetch;
425     end if;

427 when others =>
428     -- shouldnt reach here
429     next_state <= reset_state;
430 end case;
431 end if;
432 end process;

433 process(clock, reset, next_state)
434 BEGIN
435     if reset = '0' then
436         state <= reset_state;
437     elsif rising_edge(clock) then
438         state <= next_state;
439     end if;
440 end process;

441 end Behavioral;

```

Listing 11: processor/fulladder.vhd

```

-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library IEEE;
5 use IEEE.STD_LOGIC_1164.ALL;

6
7 entity fulladder is
8     Port (Ax   : in   STD_LOGIC;
9           Bx   : in   STD_LOGIC;
10          Ci   : in   STD_LOGIC;
11          Sx   : out  STD_LOGIC;
12          Co   : out  STD_LOGIC
13        );
14 end fulladder;

16
17 architecture arch_fulladder of fulladder is
18 BEGIN
19     process(Ax, Bx, Ci)
20     BEGIN
21         Sx <= (Ax XOR Bx) XOR Ci;
22         Co <= (Ax and Bx) or (Ax and Ci) OR (Bx AND Ci);
23     end process;
24 end arch_fulladder;

```

```

26 -----
28 library IEEE;
29 use IEEE.STD_LOGIC_1164.ALL;
30
31 entity fulladder8 is
32     Port (A      : in    STD_LOGIC_VECTOR( 7 downto 0);
33           B      : in    STD_LOGIC_VECTOR( 7 downto 0);
34           Cin     : in    STD_LOGIC;
35           Sum     : out   STD_LOGIC_VECTOR( 7 downto 0);
36           Cout    : out   STD_LOGIC
37           );
38 end fulladder8;
39
40 architecture arch_fulladder8 of fulladder8 is
41     component fulladder IS
42     Port (Ax      : in    STD_LOGIC;
43           Bx      : in    STD_LOGIC;
44           Ci      : in    STD_LOGIC;
45           Sx      : out   STD_LOGIC;
46           Co      : out   STD_LOGIC
47           );
48     end component;
49     signal Carry   : std_logic_vector(8 downto 0);
50 BEGIN
51     Carry(0) <= Cin;
52
53     FA0: fulladder PORT MAP(A(0), B(0), Carry(0), Sum(0), Carry(1));
54     FA1: fulladder PORT MAP(A(1), B(1), Carry(1), Sum(1), Carry(2));
55     FA2: fulladder PORT MAP(A(2), B(2), Carry(2), Sum(2), Carry(3));
56     FA3: fulladder PORT MAP(A(3), B(3), Carry(3), Sum(3), Carry(4));
57     FA4: fulladder PORT MAP(A(4), B(4), Carry(4), Sum(4), Carry(5));
58     FA5: fulladder PORT MAP(A(5), B(5), Carry(5), Sum(5), Carry(6));
59     FA6: fulladder PORT MAP(A(6), B(6), Carry(6), Sum(6), Carry(7));
60     FA7: fulladder PORT MAP(A(7), B(7), Carry(7), Sum(7), Carry(8));
61
62     Cout <= Carry(8);
63 end arch_fulladder8;
64 -----
65
66 library IEEE;
67 use IEEE.STD_LOGIC_1164.ALL;
68
69 entity fulladder16 is
70     Port (A      : in    STD_LOGIC_VECTOR( 15 downto 0);
71           B      : in    STD_LOGIC_VECTOR( 15 downto 0);
72           Cin     : in    STD_LOGIC;
73           Sum     : out   STD_LOGIC_VECTOR( 15 downto 0);
74           Cout    : out   STD_LOGIC
75           );
76 end fulladder16;
77
78 architecture arch_fulladder16 of fulladder16 is
79     component fulladder IS
80     Port (Ax      : in    STD_LOGIC;
81           Bx      : in    STD_LOGIC;
82           Ci      : in    STD_LOGIC;
83           Sx      : out   STD_LOGIC;
84           Co      : out   STD_LOGIC
85           );
86     end component;
87     signal Carry   : std_logic_vector(16 downto 0);
88 BEGIN
89     Carry(0) <= Cin;
90
91     FA0: fulladder PORT MAP(A(0), B(0), Carry(0), Sum(0), Carry(1));
92     FA1: fulladder PORT MAP(A(1), B(1), Carry(1), Sum(1), Carry(2));
93     FA2: fulladder PORT MAP(A(2), B(2), Carry(2), Sum(2), Carry(3));
94     FA3: fulladder PORT MAP(A(3), B(3), Carry(3), Sum(3), Carry(4));
95     FA4: fulladder PORT MAP(A(4), B(4), Carry(4), Sum(4), Carry(5));
96     FA5: fulladder PORT MAP(A(5), B(5), Carry(5), Sum(5), Carry(6));

```



```

98     FA6:    fulladder PORT MAP(A(6), B(6), Carry(6), Sum(6), Carry(7));
99     FA7:    fulladder PORT MAP(A(7), B(7), Carry(7), Sum(7), Carry(8));
100    FA8:    fulladder PORT MAP(A(8), B(8), Carry(8), Sum(8), Carry(9));
101    FA9:    fulladder PORT MAP(A(9), B(9), Carry(9), Sum(9), Carry(10));
102    FA10:   fulladder PORT MAP(A(10), B(10), Carry(10), Sum(10), Carry(11));
103    FA11:   fulladder PORT MAP(A(11), B(11), Carry(11), Sum(11), Carry(12));
104    FA12:   fulladder PORT MAP(A(12), B(12), Carry(12), Sum(12), Carry(13));
105    FA13:   fulladder PORT MAP(A(13), B(13), Carry(13), Sum(13), Carry(14));
106    FA14:   fulladder PORT MAP(A(14), B(14), Carry(14), Sum(14), Carry(15));
107    FA15:   fulladder PORT MAP(A(15), B(15), Carry(15), Sum(15), Carry(16));
108
109    Cout <= Carry(16);
110 end arch_fulladder16;

```

Listing 12: processor/gpr.vhd

```

-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library IEEE;
5 use IEEE.STD_LOGIC_1164.ALL;
6
7 library work;
8 use work.reg8;
9
10 entity gpr is
11     Port (clk      : in    STD_LOGIC;
12          enable    : in    STD_LOGIC;
13          SelRx      : in    STD_LOGIC_VECTOR (2 downto 0); -- The Rx output selection
14              value
15          SelRy      : in    STD_LOGIC_VECTOR (2 downto 0); -- The Ry output selection
16              value
17          SelRi      : in    STD_LOGIC_VECTOR (2 downto 0); -- The Ri input selection
18              value
19          SelIn      : in    STD_LOGIC; -- Select where the input should be from the CU
20              or CDB
21          RiCU       : in    STD_LOGIC_VECTOR (7 downto 0); -- Input from the Control
22              Unit
23          RiCDB      : in    STD_LOGIC_VECTOR (7 downto 0); -- Input from the Common Data
24              Bus
25          Rx         : out   STD_LOGIC_VECTOR (7 downto 0); -- The Rx output
26          Ry         : out   STD_LOGIC_VECTOR (7 downto 0)); -- The Ry output
27 end gpr;
28
29
30 architecture gpr_arch of gpr is
31     component reg8 IS
32         port(I      : in    std_logic_vector(7 downto 0);
33              clock   : in    std_logic;
34              enable  : in    std_logic;
35              reset   : in    std_logic;
36              Q       : out   std_logic_vector(7 downto 0)
37         );
38     end component;
39
40     signal reset: std_logic := '0';
41     signal input: std_logic_VECTOR (7 downto 0);
42     signal R0E : std_logic; -- Enable signals
43     signal R1E : std_logic;
44     signal R2E : std_logic;
45     signal R3E : std_logic;
46     signal R4E : std_logic;
47     signal R5E : std_logic;
48     signal R6E : std_logic;
49     signal R7E : std_logic;
50     signal Q0  : std_logic_VECTOR (7 downto 0);
51     signal Q1  : std_logic_VECTOR (7 downto 0);
52     signal Q2  : std_logic_VECTOR (7 downto 0);
53     signal Q3  : std_logic_VECTOR (7 downto 0);
54     signal Q4  : std_logic_VECTOR (7 downto 0);
55     signal Q5  : std_logic_VECTOR (7 downto 0);
56     signal Q6  : std_logic_VECTOR (7 downto 0);

```

```

    signal Q7 : std_logic_VECTOR (7 downto 0);
52 BEGIN
    reg_0 : reg8 port map(input, clk, R0E, reset, Q0);
54    reg_1 : reg8 port map(input, clk, R1E, reset, Q1);
    reg_2 : reg8 port map(input, clk, R2E, reset, Q2);
56    reg_3 : reg8 port map(input, clk, R3E, reset, Q3);
    reg_4 : reg8 port map(input, clk, R4E, reset, Q4);
58    reg_5 : reg8 port map(input, clk, R5E, reset, Q5);
    reg_6 : reg8 port map(input, clk, R6E, reset, Q6);
60    reg_7 : reg8 port map(input, clk, R7E, reset, Q7);

62 -- Select where the input should come from
    SelectInput: process(SelIn, RiCDB, RiCU)
64 BEGIN
    IF SelIn = '1' THEN
66         input <= RiCDB;
    ELSE
68         input <= RiCU;
    END IF;
70 END process;

72 -- Set Ri the input
    SetInput: process(clk, enable, SelRi)
74 BEGIN
    R0E <= '0';
76    R1E <= '0';
    R2E <= '0';
78    R3E <= '0';
    R4E <= '0';
80    R5E <= '0';
    R6E <= '0';
82    R7E <= '0';
    IF enable = '1' THEN
84         case SelRi IS
            WHEN "000" =>
86                 R0E <= '1';
            WHEN "001" =>
88                 R1E <= '1';
            WHEN "010" =>
90                 R2E <= '1';
            WHEN "011" =>
92                 R3E <= '1';
            WHEN "100" =>
94                 R4E <= '1';
            WHEN "101" =>
96                 R5E <= '1';
            WHEN "110" =>
98                 R6E <= '1';
            WHEN "111" =>
100                R7E <= '1';
            WHEN others =>
102                NULL; -- None of them are enabled
        end case;
104    END IF;
    end process;

106 -- Set the Rx output
108 WITH SelRx SELECT
    Rx <= Q0 WHEN "000",
110         Q1 WHEN "001",
         Q2 WHEN "010",
112         Q3 WHEN "011",
         Q4 WHEN "100",
114         Q5 WHEN "101",
         Q6 WHEN "110",
116         Q7 WHEN others;

118 -- Set the Ry output
    WITH SelRy SELECT
120    Ry <= Q0 WHEN "000",
         Q1 WHEN "001",
122         Q2 WHEN "010",
         Q3 WHEN "011",

```

```

124         Q4 WHEN "100",
           Q5 WHEN "101",
126         Q6 WHEN "110",
           Q7 WHEN others;
128
end gpr_arch;

```

Listing 13: processor/reg.vhd

```

-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library ieee;
  use ieee.std_logic_1164.all;
6
entity reg8 is
8 port(I      : in  std_logic_vector(7 downto 0);
      clock   : in  std_logic;
10      enable : in  std_logic;
      reset   : in  STD_LOGIC;
12      Q      : out std_logic_vector(7 downto 0)
      );
14 end reg8;

16 architecture behv of reg8 is
begin
18
    process(I, clock, enable, reset)
20 begin
        IF reset = '1' THEN
22             Q <= (others => '0');
        ELSIF rising_edge(clock) then
24             if enable = '1' then
                Q <= I;
26             end if;
            end if;
28
        end process;
30
end behv;
32
-----
34
library ieee;
36 use ieee.std_logic_1164.all;

38 entity reg16 is
port(I      : in  std_logic_vector(15 downto 0);
40      clock : in  std_logic;
      enable : in  std_logic;
42      reset : in  STD_LOGIC;
      Q      : out std_logic_vector(15 downto 0)
44      );
end reg16;
46
architecture behv of reg16 is
48 begin

50     process(I, clock, enable, reset)
begin
52         IF reset = '1' THEN
            Q <= (others => '0');
54         ELSIF rising_edge(clock) then
            if enable = '1' then
56                 Q <= I;
                end if;
            end if;
58
        end process;
60
end behv;
62

```

Listing 14: processor/spr.vhd

```

-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library IEEE;
  use IEEE.STD_LOGIC_1164.ALL;

6
  library work;
8 use work.reg16;

10 entity sr is
    Port (clk      : in  STD_LOGIC;
12         enable   : in  STD_LOGIC;
          reset    : in  STD_LOGIC;
14         Ri       : in  STD_LOGIC_VECTOR (15 downto 0); -- The input to the SR
          Ro       : out STD_LOGIC_VECTOR (15 downto 0)); -- The output from SR
16 end sr;

18 architecture sr_arch of sr is
    component reg16 IS
20     port(I      : in  std_logic_vector(15 downto 0);
          clock   : in  std_logic;
22         enable  : in  std_logic;
          reset   : in  STD_LOGIC;
24         Q       : out std_logic_vector(15 downto 0)
    );
26 end component;
BEGIN
28     reg_sr : reg16 port map(Ri, clk, enable, reset, Ro);
end sr_arch;
30
-----
32
  library IEEE;
34 use IEEE.STD_LOGIC_1164.ALL;

36 entity pc is
    Port (clk      : in  STD_LOGIC;
38         enable   : in  STD_LOGIC;
          reset    : in  STD_LOGIC;
40         Ri       : in  STD_LOGIC_VECTOR (15 downto 0); -- The input to the SR
          Ro       : out STD_LOGIC_VECTOR (15 downto 0)); -- The output from SR
42 end pc;

44
  architecture pc_arch of pc is
46     component reg16 IS
    port(I      : in  std_logic_vector(15 downto 0);
48         clock   : in  std_logic;
          enable  : in  std_logic;
50         reset   : in  STD_LOGIC;
          Q       : out std_logic_vector(15 downto 0)
52     );
    end component;
54 BEGIN
    reg_pc : reg16 port map(Ri, clk, enable, reset, Ro);
56 end pc_arch;

```

MMU

Listing 15: mmu/control_unit.vhd

```
1  -- Authors:
2  --      Wim Looman, Forrest McKerchar
3
4  library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
6
7  library work;
8  use work.mmu_types.all;
9
10 entity mmu_control_unit is
11     port (
12         eoc          : in  std_logic; -- High on muart has finished collecting data
13         eot          : in  std_logic; -- High on muart has finished transmitting
14         ready        : in  std_logic; -- High if the muart is ready for new transfer
15         data_read     : in  std_logic; -- High if the cpu requests a read, else write
16         data_req      : in  std_logic; -- Low to start a transfer
17         data_add_0    : in  std_logic; -- High for memory address, else IO
18         inst_req      : in  std_logic; -- Low to start a transfer
19         fr           : in  std_logic; -- Input headers fetch request bit
20         inst_or_data_in : in  std_logic; -- Input headers inst or data bit
21         rw           : in  std_logic; -- Input headers read/write bit
22         write         : out std_logic; -- Pulled high to start muart writing data
23         inst_or_data_out : out std_logic; -- Output headers inst or data bit
24         inst_ack      : out std_logic; -- Idles high, pulled low when data ready
25         data_ack      : inout std_logic; -- Idles 'Z', high when data not ready,
26             pulled low when data ready
27         muart_input   : out muart_input_state; -- Signal connected to muart input
28         muart_output  : out muart_output_state; -- Signal connected to muart output
29         clk           : in  std_logic
30     );
31 end mmu_control_unit;
32
33 architecture mmu_control_unit_arch of mmu_control_unit is
34     component data_control_unit is
35         port (
36             eoc          : in  std_logic; -- High on muart has finished collecting data
37             eot          : in  std_logic; -- High on muart has finished transmitting
38             ready        : in  std_logic; -- High if the muart is ready for new transfer
39             data_read     : in  std_logic; -- High if the cpu requests a read, else write
40             data_req      : in  std_logic; -- Low to start a transfer
41             data_add_0    : in  std_logic; -- High for memory address, else IO
42             write         : out std_logic; -- Pulled high to start muart writing data.
43             data_ack      : inout std_logic; -- Idles 'Z', high when data not ready, pulled
44                 low when data ready
45             muart_input   : out muart_input_state; -- Signal connected to muart input
46             muart_output  : out muart_output_state; -- Signal connected to muart output
47             clk           : in  std_logic
48         );
49     end component;
50
51     component inst_control_unit is
52         port (
53             eoc          : in  std_logic; -- High on muart has finished collecting data
54             eot          : in  std_logic; -- High on muart has finished transmitting
55             ready        : in  std_logic; -- High if the muart is ready for new transfer
56             inst_req      : in  std_logic; -- Low to start a transfer
57             write         : out std_logic; -- Pulled high to start muart writing data
58             inst_or_data_in : out std_logic; -- Output headers inst or data bit
59             inst_ack      : out std_logic; -- Idles high, pulled low when data ready
60             muart_input   : out muart_input_state; -- Signal connected to muart input
61             muart_output  : out muart_output_state; -- Signal connected to muart output
62             clk           : in  std_logic
63         );
64     end component;
65
66     signal data_write, inst_write, inst_inst_or_data_out : std_logic;
67     signal data_muart_input, inst_muart_input : muart_input_state;
68     signal data_muart_output, inst_muart_output : muart_output_state;
```

```

67 begin
    data_cu : data_control_unit port map (
69     eoc,
        eot,
71     ready,
        data_read,
73     data_req,
        data_add_0,
75     data_write,
        data_ack,
77     data_muart_input,
        data_muart_output,
79     clk
    );
81 inst_cu : inst_control_unit port map (
    eoc,
83     eot,
        ready,
85     inst_req,
        inst_write,
87     inst_inst_or_data_out,
        inst_ack,
89     inst_muart_input,
        inst_muart_output,
91     clk
    );
93
    inst_or_data_out <= inst_inst_or_data_out ;
95 write          <= inst_write or data_write;
    muart_input   <= inst_muart_input when inst_inst_or_data_out = '1' else
97     data_muart_input;
    muart_output <= inst_muart_output when inst_inst_or_data_out = '1' else
99     data_muart_output;
end mmu_control_unit_arch;

```

Listing 16: mmu/data_control_unit.vhd

```

-- Authors:
2 --      Wim Looman, Forrest McKerchar

4 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

6
library work;
8 use work.mmu_types.all;

10 entity data_control_unit is
    port (
12         eoc          : in  std_logic; -- High on muart has finished collecting data
        eot          : in  std_logic; -- High on muart has finished transmitting
14         ready       : in  std_logic; -- High if the muart is ready for new transfer
        data_read    : in  std_logic; -- High if the cpu requests a read, else write
16         data_req    : in  std_logic; -- Low to start a transfer
        data_add_0   : in  std_logic; -- High for memory address, else IO
18         write       : out std_logic; -- Pulled high to start muart writing data.
        data_ack     : inout std_logic; -- Idles 'Z', high when data not ready, pulled
        low when data ready
20         muart_input  : out muart_input_state; -- Signal connected to muart input
        muart_output  : out muart_output_state; -- Signal connected to muart output
22         clk         : in  std_logic
    );
24 end data_control_unit;

26 architecture data_control_unit_arch of data_control_unit is
    type m_state_type is (
28         idle,
        send_header, send_add_high, send_add_low, send_data,
30         get_header, get_add_high, get_add_low, get_data,
        finished
32     );
    type state_type      is (idle, get_data, wait_clear);
34    type read_state_type is (idle, wait_data, read_data, pause, finished);

```

```

type transmit_state_type is (idle, set_data, trans_data, pause, finished);
36
signal state,                next_state                : state_type                := idle;
38 signal get_state,          next_get_state            : m_state_type                := idle;
signal reader_state,         next_reader_state         : read_state_type            := idle;
40 signal transmitter_state,  next_transmitter_state    : transmit_state_type        := idle;
begin
42 data_fsm : process(state, data_req, clk) begin
    if (rising_edge(clk)) then
44         case state is
            when idle =>
46             if (data_req = '0' and data_add_0 = '1') then
                 next_state <= get_data;
48             end if;

50             when get_data =>
                 if (get_state = finished) then
52                     next_state <= wait_clear;
                 end if;

54                 when wait_clear =>
56                     if (data_req = '1') then
                         next_state <= idle;
58                     end if;

60                     when others =>
                         NULL;
62                 end case;
            end if;
64 end process data_fsm;

66 get_data_fsm : process(state, clk) begin
    if rising_edge(clk) then
68         if state = get_data then
            case get_state is
70                 when idle =>
                     next_get_state <= send_header;
72

                 when send_header =>
74                     if transmitter_state = finished then
                         next_get_state <= send_add_low;
76                     end if;

78                     when send_add_low =>
                         if transmitter_state = finished then
80                             next_get_state <= send_add_high;
                         end if;

82                     when send_add_high =>
84                         if transmitter_state = finished then
                             if data_read = '1' then
86                                 next_get_state <= get_header;
                             else
88                                 next_get_state <= send_data;
                             end if;
90                         end if;

92                     when send_data =>
                         if transmitter_state = finished then
94                             next_get_state <= finished;
                         end if;

96                     when get_header =>
98                         if reader_state = finished then
                             next_get_state <= get_add_low;
100                        end if;

102                     when get_add_low =>
                         if reader_state = finished then
104                             next_get_state <= get_add_high;
                         end if;

106                     when get_add_high =>

```

```

108         if reader_state = finished then
109             next_get_state <= get_data;
110         end if;

112     when get_data =>
113         if reader_state = finished then
114             next_get_state <= finished;
115         end if;

116     when finished =>
117         next_get_state <= idle;

120     when others =>
121         NULL;
122     end case;
123 end if;
124 end if;
125 end process get_data_fsm;

126 transmit_fsm : process(clk, get_state, transmitter_state, eot) begin
127     if rising_edge(clk) then
128         if ((get_state = send_header) or
129             (get_state = send_add_low) or
130             (get_state = send_add_high) or
131             (get_state = send_data)) then
132             case transmitter_state is
133             when idle =>
134                 if ready = '1' and eot = '0' then
135                     next_transmitter_state <= set_data;
136                 end if;

138             when set_data =>
139                 next_transmitter_state <= trans_data;

142             when trans_data =>
143                 next_transmitter_state <= pause;

144             when pause =>
145                 if eot = '1' then
146                     next_transmitter_state <= finished;
147                 end if;

150             when finished =>
151                 next_transmitter_state <= idle;

152             when others =>
153                 NULL;
154             end case;
155         end if;
156     end if;
157 end process transmit_fsm;

158 read_fsm : process(clk, get_state, reader_state, eoc) begin
159     if rising_edge(clk) then
160         if ((get_state = get_header) or
161             (get_state = get_add_low) or
162             (get_state = get_add_high) or
163             (get_state = get_data)) then
164             case reader_state is
165             when idle =>
166                 next_reader_state <= wait_data;

170             when wait_data =>
171                 if eoc = '1' then
172                     next_reader_state <= read_data;
173                 end if;

174             when read_data =>
175                 next_reader_state <= pause;

176             when pause =>
177                 if eoc = '0' then
178                     next_reader_state <= finished;

```



```

        end if;
182
        when finished =>
184            next_reader_state <= idle;

186            when others =>
                NULL;
188            end case;
        end if;
190    end process read_fsm;

192    switch_states : process(
194        clk,
        next_state,
196        next_get_state,
        next_reader_state,
198        next_transmitter_state
    ) begin
200        if rising_edge(clk) then
            state <= next_state;
202            get_state <= next_get_state;
            reader_state <= next_reader_state;
204            transmitter_state <= next_transmitter_state;
        end if;
206    end process switch_states;

208    -- Outputs
    with state select
210        data_ack <= '1' when wait_clear,
                                'Z' when idle,
212                                '0' when others;

214    with transmitter_state select
        write <= '1' when trans_data,
216                '0' when others;

218    uart_input <= idle          when transmitter_state /= set_data      else
        idle                    when transmitter_state /= trans_data     else
220        header                  when get_state         = send_header    else
        data_add_high when get_state         = send_add_high else
222        data_add_low when get_state         = send_add_low  else
        data_data    when get_state         = send_data      else
224        idle;

226    uart_output <= clear_data when state = idle      else
        idle            when reader_state /= read_data else
228        header         when get_state = get_header else
        data_data       when get_state = get_data    else
230        idle;
    end data_control_unit_arch;

```

Listing 17: mmu/header_builder.vhd

```

1  -- Author:
   --      Forrest McKerchar
3
   -- builds a header to feed into the RS-232 link
5
   library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;

9  library work;

11 entity header_builder is
    port (
13        read_write : in  std_logic; -- 1 = read, 0 = write
        inst_data   : in  std_logic; -- 1 = inst, 0 = data
15        header     : out std_logic_vector(7 downto 0)
    );
17 end header_builder;

```

```

19 architecture header_builder_arch of header_builder is
begin
21   header(7) <= read_write or inst_data; -- reading from or writing to
                                         -- memory? (can't write
                                         -- instructions)
23   header(6) <= '0'; -- reserved
25   header(5) <= '0'; -- reserved
   header(4) <= '0'; -- reserved
27   header(3) <= '0'; -- diagnostic
   header(2) <= '0'; -- diagnostic;
29   header(1) <= '0'; -- 1 if data is being retrieved from RS-232 link
   header(0) <= inst_data; -- instruction data or data data?
31 end header_builder_arch;

```

Listing 18: mmu/header_decoder.vhd

```

-- Author:
2 --      Forrest McKerchar

4 -- decodes a header received from the RS-232 link

6 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

8
library work;
10
entity header_decoder is
12   port (
       read_write      : out  std_logic; -- 1 = read, 0 = write
14       fetch_request : out  std_logic;
       inst_data       : out  std_logic; -- 1 = inst, 0 = data
16       header        : in  std_logic_vector(7 downto 0)
   );
18 end header_decoder;

20 architecture header_decoder_arch of header_decoder is
begin
22   read_write <= header(7); -- reading or writing? (should be 1 in this case)
       fetch_request <= header(1); -- fetch request? (should be 1 in this case)
24   inst_data <= header(0); -- instruction data or data data?
end header_decoder_arch;

```

Listing 19: mmu/inst_control_unit.vhd

```

-- Authors:
2 --      Wim Looman, Forrest McKerchar

4 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

6
library work;
8 use work.mmu_types.all;

10 entity inst_control_unit is
   port (
12       eoc           : in  std_logic; -- High on muart has finished collecting data
       eot           : in  std_logic; -- High on muart has finished transmitting
14       ready        : in  std_logic; -- High if the muart is ready for new transfer
       inst_req      : in  std_logic; -- Low to start a transfer
16       write        : out std_logic; -- Pulled high to start muart writing data
       inst_or_data  : out std_logic; -- Output headers inst or data bit
18       inst_ack     : out std_logic; -- Idles high, pulled low when data ready
       muart_input   : out muart_input_state; -- Signal connected to muart input
20       muart_output  : out muart_output_state; -- Signal connected to muart output
       clk           : in  std_logic
   );
22 end inst_control_unit;

24
architecture inst_control_unit_arch of inst_control_unit is
26   type m_state_type is (

```

```

idle,
28  send_header,    send_add_high, send_add_low,
   get_header,    get_add_high,  get_add_low,
30  get_data_high, get_data_low,  finished
);
32  type state_type      is (idle, get_data, wait_clear);
   type read_state_type is (idle, wait_data, read_data, pause, finished);
34  type transmit_state_type is (idle, set_data, trans_data, pause, finished);

36  signal state,          next_state          : state_type      := idle;
   signal get_state,      next_get_state      : m_state_type    := idle;
38  signal reader_state,   next_reader_state   : read_state_type   := idle;
   signal transmitter_state, next_transmitter_state : transmit_state_type := idle;
40 begin
   inst_fsm : process(state, inst_req, clk) begin
42     case state is
         when idle =>
44         if (inst_req = '0') then
             next_state <= get_data;
46         end if;

48         when get_data =>
             if (get_state = finished) then
                 next_state <= wait_clear;
50             end if;

52         when wait_clear =>
             if (inst_req = '1') then
                 next_state <= idle;
54             end if;

56         when others =>
             NULL;
60     end case;
   end process inst_fsm;

62   get_inst_fsm : process(state, clk) begin
44     if state = get_data then
         case get_state is
66         when idle =>
             next_get_state <= send_header;

68         when send_header =>
70         if transmitter_state = finished then
             next_get_state <= send_add_low;
72         end if;

74         when send_add_low =>
             if transmitter_state = finished then
                 next_get_state <= send_add_high;
76             end if;

78         when send_add_high =>
80         if transmitter_state = finished then
             next_get_state <= get_header;
82         end if;

84         when get_header =>
             if reader_state = finished then
                 next_get_state <= get_add_low;
86             end if;

88         when get_add_low =>
90         if reader_state = finished then
             next_get_state <= get_add_high;
92         end if;

94         when get_add_high =>
             if reader_state = finished then
                 next_get_state <= get_data_low;
96             end if;

98         when get_data_low =>

```

```

100         if reader_state = finished then
101             next_get_state <= get_data_high;
102         end if;

104     when get_data_high =>
105         if reader_state = finished then
106             next_get_state <= finished;
107         end if;

108     when finished =>
109         next_get_state <= idle;

112     when others =>
113         NULL;
114     end case;
115 end if;
116 end process get_inst_fsm;

118 transmit_fsm : process(clk, get_state, transmitter_state, eot) begin
119     if ((get_state = send_header) or
120         (get_state = send_add_low) or
121         (get_state = send_add_high)) then
122     case transmitter_state is
123         when idle =>
124             if ready = '1' and eot = '0' then
125                 next_transmitter_state <= set_data;
126             end if;

128         when set_data =>
129             next_transmitter_state <= trans_data;

130         when trans_data =>
131             next_transmitter_state <= pause;

132         when pause =>
133             if eot = '1' then
134                 next_transmitter_state <= finished;
135             end if;

136         when finished =>
137             next_transmitter_state <= idle;

142         when others =>
143             NULL;
144         end case;
145     end if;
146 end process transmit_fsm;

148 read_fsm : process(clk, get_state, reader_state, eoc) begin
149     if ((get_state = get_header) or
150         (get_state = get_add_low) or
151         (get_state = get_add_high) or
152         (get_state = get_data_low) or
153         (get_state = get_data_high)) then
154     case reader_state is
155         when idle =>
156             next_reader_state <= wait_data;

158         when wait_data =>
159             if eoc = '1' then
160                 next_reader_state <= read_data;
161             end if;

162         when read_data =>
163             next_reader_state <= pause;

164         when pause =>
165             if eoc = '0' then
166                 next_reader_state <= finished;
167             end if;

168         when finished =>
169             next_reader_state <= idle;

```

```

174         when others =>
175             NULL;
176         end case;
177     end if;
178 end process read_fsm;

180 switch_states : process(
181     clk,
182     next_state,
183     next_get_state,
184     next_reader_state,
185     next_transmitter_state) begin
186     if rising_edge(clk) then
187         state <= next_state;
188         get_state <= next_get_state;
189         reader_state <= next_reader_state;
190         transmitter_state <= next_transmitter_state;
191     end if;
192 end process switch_states;

194 -- Outputs
195 with state select
196     inst_ack <= '1' when wait_clear,
197               '0' when others;

198
199 with state select
200     inst_or_data <= '0' when idle,
201                   '1' when others;

202
203 with transmitter_state select
204     write <= '1' when trans_data,
205            '0' when others;

206
207
208 uart_input <= idle          when transmitter_state /= set_data      else
209                    idle      when transmitter_state /= trans_data   else
210                    header     when get_state        = send_header   else
211                    inst_add_high when get_state      = send_add_high else
212                    inst_add_low when get_state      = send_add_low  else
213                    idle;

214
215 uart_output <= idle          when reader_state /= read_data      else
216                    header     when get_state    = get_header     else
217                    inst_data_high when get_state = get_data_high  else
218                    inst_data_low when get_state = get_data_low   else
219                    idle;

220 end inst_control_unit_arch;

```

Listing 20: mmu/mmu.vhd

```

-- Authors:
2 --      Wim Looman, Forrest McKerchar

4 library IEEE;
5 use IEEE.STD_LOGIC_1164.ALL;

6
7 library work;
8 use work.mmu_types.all;
9 use work.mmu_control_unit;
10 use work.header_builder;
11 use work.header_decoder;
12 use work.reg8;

13
14 use work.minimal_uart_core;

15
16 entity mmu_main is
17     port (
18         -- instruction bus
19         inst_add : in  std_logic_vector(11 downto 0); -- Address lines.
20         inst_data : out std_logic_vector(15 downto 0); -- Data lines.

```

```

    inst_req : in std_logic; -- Pulled low to request bus
    usage.
22    inst_ack : out std_logic; -- Pulled high to inform of
    request completion.
    -- data bus
24    data_add : in std_logic_vector(15 downto 0); -- Address lines.
    data_line : inout std_logic_vector(7 downto 0); -- Data lines.
26    data_read : in std_logic; -- High for a read request,
    low for a write request.
    data_req : in std_logic; -- Pulled low to request bus
    usage.
28    data_ack : inout std_logic; -- Pulled high to inform of
    request completion.
    -- extras
30    clk : in std_logic;
    receive_pin : in std_logic;
32    transfer_pin : out std_logic
);
34 end mmu_main;

36 architecture mmu_arch of mmu_main is
    component mmu_control_unit is
38    port (
        eoc : in std_logic; -- High on muart has finished collecting
        data
40        eot : in std_logic; -- High on muart has finished transmitting
        ready : in std_logic; -- High if the muart is ready for new
        transfer
42        data_read : in std_logic; -- High if the cpu requests a read, else
        write
        data_req : in std_logic; -- Low to start a transfer
44        data_add_0 : in std_logic; -- High for memory address, else IO
        inst_req : in std_logic; -- Low to start a transfer
46        fr : in std_logic; -- Input headers fetch request bit
        inst_or_data_in : in std_logic; -- Input headers inst or data bit
48        rw : in std_logic; -- Input headers read/write bit
        write : out std_logic; -- Pulled high to start muart writing data
50        inst_or_data_out : out std_logic; -- Output headers inst or data bit
        inst_ack : out std_logic; -- Idles high, pulled low when data ready
52        data_ack : inout std_logic; -- Idles 'Z', high when data not ready,
        pulled low when data ready
        muart_input : out muart_input_state; -- Signal connected to muart input
54        muart_output : out muart_output_state; -- Signal connected to muart
        output
        clk : in std_logic
    );
56 end component;

58 component header_builder is
60    port (
        read_write : in std_logic; -- 1 = read, 0 = write
62        inst_data : in std_logic; -- 1 = inst, 0 = data
        header : out std_logic_vector(7 downto 0)
    );
64 end component;

66 component header_decoder is
68    port (
        read_write : out std_logic; -- 1 = read, 0 = write
70        fetch_request : out std_logic;
        inst_data : out std_logic; -- 1 = inst, 0 = data
72        header : in std_logic_vector(7 downto 0)
    );
74 end component;

76 component minimal_uart_core is
    port(
78        clock : in std_logic;
        eoc : out std_logic;
80        outp : inout std_logic_vector(7 downto 0) := "ZZZZZZZZ";
        rxd : in std_logic;
82        txd : out std_logic;
        eot : out std_logic;

```

```

84     inp  : in    std_logic_vector(7 downto 0);
      ready : out   std_logic;
86     wr   : in    std_logic
    );
88 end component;

90 component reg8 IS
    port(
92         I      : in    std_logic_vector(7 downto 0);
          clock  : in    std_logic;
94         enable : in    std_logic;
          reset  : in    std_logic;
96         Q      : out   std_logic_vector(7 downto 0)
    );
98 end component;

100
102 signal eoc      : std_logic;
104 signal eot      : std_logic;
106 signal ready    : std_logic;
108 signal fr       : std_logic;
110 signal inst_or_data_in : std_logic;
112 signal rw       : std_logic;

114 signal write     : std_logic;
116 signal inst_or_data_out : std_logic;
118 signal muart_input  : muart_input_state;
120 signal muart_output : muart_output_state;

122 signal muart_out : std_logic_vector(7 downto 0);
124 signal muart_in  : std_logic_vector(7 downto 0);
126 signal header_in : std_logic_vector(7 downto 0);
128 signal header_out : std_logic_vector(7 downto 0);
130 signal inst_data_high_enable : std_logic;
132 signal inst_data_low_enable : std_logic;
134 signal data_data_enable : std_logic;
136 signal data_line_tri : std_logic_vector(7 downto 0);

138 begin
140 muart : minimal_uart_core port map (
142     clk,
144     eoc,
146     muart_out,
148     receive_pin,
150     transfer_pin,
152     eot,
154     muart_in,
156     ready,
158     write
    );
160 cu : mmu_control_unit port map (
162     eoc,
164     eot,
166     ready,
168     data_read,
170     data_req,
172     data_add(0),
174     inst_req,
176     fr,
178     inst_or_data_in,
180     rw,
182     write,
184     inst_or_data_out,
186     inst_ack,
188     data_ack,
190     muart_input,
192     muart_output,
194     clk
    );
196 hb : header_builder port map (
198     data_read,
200     inst_or_data_out,
202     header_out

```

```

);
158 hd : header_decoder port map (
    rw,
160    fr,
    inst_or_data_in,
162    header_in
);
164 idh : reg8 port map (
    muart_out,
166    clk,
    inst_data_high_enable,
168    '0',
    inst_data(15 downto 8)
170 );
172 idl : reg8 port map (
    muart_out,
    clk,
174    inst_data_low_enable,
    '0',
176    inst_data(7 downto 0)
);
178 dd : reg8 port map (
    muart_out,
180    clk,
    data_data_enable,
182    '0',
    data_line_tri
184 );

186 with muart_input select
    muart_in <= header_out when header,
188                "0000" & inst_add(11 downto 8) when inst_add_high,
                inst_add(7 downto 0) when inst_add_low,
190                '0' & data_add(15 downto 9) when data_add_high,
                data_add(8 downto 1) when data_add_low,
192                data_line when data_data,
                (others => '0') when others;

194
route_output : process(muart_output, muart_out) begin
196     header_in <= (others => '0');
    inst_data_high_enable <= '0';
198     inst_data_low_enable <= '0';
    data_data_enable <= '0';
200     case muart_output is
        when header =>
202         header_in <= muart_out;

204         when inst_data_high =>
            inst_data_high_enable <= '1';

206         when inst_data_low =>
            inst_data_low_enable <= '1';

208         when data_data =>
            data_data_enable <= '1';
210         when others =>
            NULL;
212     end case;
214 end process;

216
data_line <= data_line_tri when data_add(0) = '1' and data_read = '1' else
218     (others => 'Z');

220 end mmu_arch;

```

Listing 21: mmu/mmu_types.vhd

```

-- Authors:
2 --      Wim Looman, Forrest McKerchar

4 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```



```

6
package mmu_types is
8   type uart_input_state is (header, inst_add_high, inst_add_low, data_add_high,
      data_add_low, data_data, idle);
      type uart_output_state is (header, inst_data_high, inst_data_low, data_data,
      clear_data, idle);
10 end mmu_types;

```

Listing 22: mmu/muart/BRG.vhd

```

--*****
2  --* Minimal UART ip core *
--* Author: Arao Hayashida Filho      arao@medinovacao.com.br *
4  --* *
--*****
6  --* *
--* Copyright (C) 2009 Arao Hayashida Filho *
8  --* *
--* This source file may be used and distributed without *
12 --* restriction provided that this copyright statement is not *
--* removed from the file and that any derivative work contains *
12 --* the original copyright notice and the associated disclaimer. *
--* *
14 --* This source file is free software; you can redistribute it *
--* and/or modify it under the terms of the GNU Lesser General *
16 --* Public License as published by the Free Software Foundation; *
--* either version 2.1 of the License, or (at your option) any *
18 --* later version. *
--* *
20 --* This source is distributed in the hope that it will be *
--* useful, but WITHOUT ANY WARRANTY; without even the implied *
22 --* warranty of MERCHANTABILITY or FITNESS FOR A PARTICULAR *
--* PURPOSE. See the GNU Lesser General Public License for more *
24 --* details. *
--* *
26 --* You should have received a copy of the GNU Lesser General *
--* Public License along with this source; if not, download it *
28 --* from http://www.opencores.org/lgpl.shtml *
--* *
30 --*****

32 library ieee;
use ieee.std_logic_1164.all;
34 use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned."+";
36
entity br_generator is
38   generic (divider_width: integer := 16);
   port (
40     clock      : in  std_logic;
      rx_enable  : in  std_logic;
42     clk_txd    : out std_logic;
      tx_enable  : in  std_logic;
44     clk_serial : out std_logic
   );
46 end br_generator;

48 architecture principal of br_generator is
   -- change the following constant to your desired baud rate
50   -- one hz equal to one bit per second
   signal count_brg      : std_logic_vector(divider_width - 1 downto 0) := (others =>
      '0');
52   signal count_brg_txd  : std_logic_vector(divider_width - 1 downto 0) := (others =>
      '0');
   constant brdvd        : std_logic_vector(divider_width - 1 downto 0) := x"0516";
      -- 38400 bps @ 50MHz

54   begin
56     txd : process (clock)
       begin
58       if (rising_edge(clock)) then
         if (count_brg_txd = brdvd) then

```

```

60         clk_txd         <= '1';
        count_brg_txd <= (others => '0');
62     elsif (tx_enable = '1') then
        clk_txd         <= '0';
        count_brg_txd <= count_brg_txd + 1;
        else
66         clk_txd         <= '0';
        count_brg_txd <= (others => '0');
68     end if;
    end if;
70 end process txd;

72 rxd : process (clock)
begin
74     if (rising_edge(clock)) then
        if (count_brg=brdvd) then
76         count_brg <= (others => '0');
        clk_serial <= '1';
78     elsif (rx_enable = '1') then
        count_brg <= count_brg+1;
80         clk_serial <= '0';
        else
82         count_brg <= '0' & brdvd(divider_width - 1 downto 1);
        clk_serial <= '0';
84     end if;
    end if;
86 end process rxd;
end principal;

```

Listing 23: mmu/muart/serial.vhd

```

1  --*****
2  --* Minimal UART ip core *
3  --* Author: Arao Hayashida Filho          arao@medinovacao.com.br *
4  --* * *
5  --*****
6  --* *
7  --* Copyright (C) 2009 Arao Hayashida Filho *
8  --* *
9  --* This source file may be used and distributed without *
10 --* restriction provided that this copyright statement is not *
11 --* removed from the file and that any derivative work contains *
12 --* the original copyright notice and the associated disclaimer. *
13 --* *
14 --* This source file is free software; you can redistribute it *
15 --* and/or modify it under the terms of the GNU Lesser General *
16 --* Public License as published by the Free Software Foundation; *
17 --* either version 2.1 of the License, or (at your option) any *
18 --* later version. *
19 --* *
20 --* This source is distributed in the hope that it will be *
21 --* useful, but WITHOUT ANY WARRANTY; without even the implied *
22 --* warranty of MERCHANTABILITY or FITNESS FOR A PARTICULAR *
23 --* PURPOSE. See the GNU Lesser General Public License for more *
24 --* details. *
25 --* *
26 --* You should have received a copy of the GNU Lesser General *
27 --* Public License along with this source; if not, download it *
28 --* from http://www.opencores.org/lgpl.shtml *
29 --* *
30 --*****
31
32 library IEEE;
33 use IEEE.STD_LOGIC_1164.ALL;

34
35 entity minimal_uart_core is
    port(
36         clock : in      std_logic;
37         eoc   : out     std_logic;
38         outp  : inout   std_logic_vector(7 downto 0) := "ZZZZZZZZ";
39         rxd   : in      std_logic;
40         txd   : out     std_logic;

```

```

    eot      : out      std_logic;
43    inp      : in       std_logic_vector(7 downto 0);
    ready    : out      std_logic;
45    wr       : in       std_logic
);
47 end minimal_uart_core;

49 architecture principal of minimal_uart_core is
    type state is (s0, s1, s2, s3, s4, s5, s6, s7, s8, s9);
51    signal clk_serial      : std_logic := '0';
    signal start            : std_logic := '0';
53    signal eocs, eoc1, eoc2 : std_logic := '0';
    signal rx_ck_enable     : std_logic := '0';
55    signal receiving       : std_logic := '0';
    signal transmitting     : std_logic := '0';
57    signal clk_txd         : std_logic := '0';
    signal txds             : std_logic := '1';
59    signal eots            : std_logic := '0';
    signal inpl             : std_logic_vector(7 downto 0) := x"00";
61    signal data            : std_logic_vector(7 downto 0) := x"00";
    signal atual_state, next_state, atual_state_txd, next_state_txd : state := s0;
63    signal tx_enable       : std_logic := '0';
    signal tx_ck_enable     : std_logic := '0';
65
    component br_generator
67    port (
        clock      : in  std_logic;
69        rx_enable  : in  std_logic;
        clk_txd    : out std_logic;
71        tx_enable  : in  std_logic;
        clk_serial : out std_logic
    );
73 end component;
75
begin
77    ready <= not(tx_enable);
    brg : br_generator port map (clock, rx_ck_enable, clk_txd, tx_ck_enable,
        clk_serial);
79    rx_ck_enable <= start or receiving;
    tx_ck_enable <= tx_enable or transmitting;
81
    start_detect : process(rxd, eocs)
83    begin
        if (eocs = '1') then
85            start <= '0';
        elsif (falling_edge(rxd)) then
87            start <= '1';
        end if;
89    end process start_detect;

91    rxd_states : process (clk_serial)
    begin
93        if (rising_edge(clk_serial)) then
            atual_state <= next_state;
95        end if;
    end process rxd_states;

97    rxd_state_machine : process(start, atual_state)
99    begin
        if (start = '1' or receiving = '1') then
101            case atual_state is
                when s0 =>
103                eocs <= '0';
                if (start = '1') then
105                    next_state <= s1;
                    receiving <= '1';
107                else
                    next_state <= s0;
                    receiving <= '0';
109                end if;
            end if;
111
            when s1 =>
113                receiving <= '1';

```

```

115         eocs          <= '0';
        next_state <= s2;

117     when s2 =>
        receiving <= '1';
119         eocs          <= '0';
        next_state <= s3;

121     when s3 =>
        receiving <= '1';
123         eocs          <= '0';
        next_state <= s4;

125     when s4 =>
        receiving <= '1';
127         eocs          <= '0';
        next_state <= s5;

129     when s5 =>
        receiving <= '1';
131         eocs          <= '0';
        next_state <= s6;

133     when s6 =>
        receiving <= '1';
135         eocs          <= '0';
        next_state <= s7;

137     when s7 =>
        receiving <= '1';
139         eocs          <= '0';
        next_state <= s8;

141     when s8 =>
        receiving <= '1';
143         eocs          <= '0';
        next_state <= s9;

145     when s9 =>
        receiving <= '1';
147         eocs          <= '1';
        next_state <= s0;

149     when others =>
        null;

151     end case;
153 end if;
155 end process rxd_state_machine;

157 rxd_shift : process(clk_serial)
159 begin
        if (rising_edge(clk_serial)) then
161             if (eocs = '0') then
163                 data <= rxd & data(7 downto 1);
165             end if;
167         end if;
169     end process rxd_shift;

171 process (clock)
173 begin
        if (rising_edge(clock)) then
175             eoc <= eocs;
177         end if;
        end process;

179 process(atual_state)
181 begin
        if (atual_state=s9) then
183             outp <= data;
        end if;
185     end process;

```

```

187   txd_states : process(clk_txd)
188   begin
189       if (rising_edge(clk_txd)) then
190           atual_state_txd <= next_state_txd;
191       end if;
192   end process txd_states;
193
194   txd_state_machine : process(atual_state_txd, tx_enable)
195   begin
196       case atual_state_txd is
197           when s0 =>
198               inpl <= inp;
199               eots <= '0';
200               if (tx_enable = '1') then
201                   txds <= '0';
202                   transmitting <= '1';
203                   next_state_txd <= s1;
204               else
205                   txds <= '1';
206                   transmitting <= '0';
207                   next_state_txd <= s0;
208               end if;
209
210           when s1 =>
211               txds <= inpl(0);
212               eots <= '0';
213               transmitting <= '1';
214               next_state_txd <= s2;
215
216           when s2 =>
217               txds <= inpl(1);
218               eots <= '0';
219               transmitting <= '1';
220               next_state_txd <= s3;
221
222           when s3 =>
223               txds <= inpl(2);
224               eots <= '0';
225               transmitting <= '1';
226               next_state_txd <= s4;
227
228           when s4 =>
229               txds <= inpl(3);
230               eots <= '0';
231               transmitting <= '1';
232               next_state_txd <= s5;
233
234           when s5 =>
235               txds <= inpl(4);
236               eots <= '0';
237               transmitting <= '1';
238               next_state_txd <= s6;
239
240           when s6 =>
241               txds <= inpl(5);
242               eots <= '0';
243               transmitting <= '1';
244               next_state_txd <= s7;
245
246           when s7 =>
247               txds <= inpl(6);
248               eots <= '0';
249               transmitting <= '1';
250               next_state_txd <= s8;
251
252           when s8 =>
253               txds <= inpl(7);
254               eots <= '0';
255               transmitting <= '1';
256               next_state_txd <= s9;
257
258           when s9 =>
259               txds <= '1';

```

```

261         eots          <= '1';
        transmitting    <= '1';
        next_state_txd <= s0;
263
        when others =>
265             null;
267
        end case;
    end process txd_state_machine;
269
    tx_start:process (clock, wr, eots)
271    begin
        if (eots = '1') then
273             tx_enable <= '0';
            elsif (falling_edge(clock)) then
275                 if (wr = '1') then
                    tx_enable <= '1';
277                 end if;
            end if;
279    end process tx_start;
281
    eot<=eots;
283
    process (clock)
    begin
285         if (rising_edge(clock)) then
            txd <= txds;
287         end if;
    end process;
289
    end principal ;

```

Test Benchs

Listing 24: processor/alu_tb.vhd

```
-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

6
-- A testbench has no ports.
8 entity alu_tb is
    end alu_tb;

10
architecture behav of alu_tb is
12 -- Declaration of the component that will be instantiated.
    component alu
14     Port (f      : in      STD_LOGIC_VECTOR (3 downto 0); -- Function (opcode)
           rx      : in      STD_LOGIC_VECTOR (7 downto 0); -- Input x (Rx)
16     ry      : in      STD_LOGIC_VECTOR (7 downto 0); -- Input y (Ry)
           ro      : out     STD_LOGIC_VECTOR (7 downto 0); -- Output Normaly (Ry)
18     Cin      : in      STD_LOGIC; -- Carry in
           sr      : out     STD_LOGIC_VECTOR (15 downto 0)); -- Status register out Z(0),
                           C(1), N(2)
20 end component;
-- Specifies which entity is bound with the component.
22 for alu_0: alu use entity work.alu;
    signal f      : STD_LOGIC_VECTOR (3 downto 0);
24    signal rx, ry, ro : STD_LOGIC_VECTOR (7 downto 0);
    signal Cin      : STD_LOGIC;
26    signal sr      : STD_LOGIC_VECTOR (15 downto 0);
begin
28 -- Component instantiation.
    alu_0: alu port map (f => f, rx => rx, ry => ry, ro => ro, Cin => Cin, sr => sr);
30
-- This process does the real job.
32 process
    type pattern_type is record
34         f      : STD_LOGIC_VECTOR (3 downto 0);
         rx, ry      : STD_LOGIC_VECTOR (7 downto 0);
36         ro      : STD_LOGIC_VECTOR (7 downto 0);
         Cin      : STD_LOGIC;
38         sr      : STD_LOGIC_VECTOR (15 downto 0);
    end record;
40 -- The patterns to apply.
    type pattern_array is array (natural range <>) of pattern_type;
42 constant patterns : pattern_array :=
-- f      rx      ry      ro      Cin      sr
44 (( "0001", "00000000", "00000000", "00000000", '0', "0000000000000001"), --AND tests
    - 1ns
    ( "0001", "00000001", "00000001", "00000001", '0', "0000000000000000"), --AND tests
46 ( "0001", "00000000", "00000001", "00000000", '0', "0000000000000001"), --AND tests
    ( "0001", "10101010", "10101010", "10101010", '0', "0000000000000100"), --AND tests
48 ( "0001", "01010101", "01010101", "01010101", '0', "0000000000000000"), --AND tests
    - 5ns
    ( "0001", "11111111", "00000000", "00000000", '0', "0000000000000001"), --AND tests
50 ( "0001", "11111111", "11111111", "11111111", '0', "0000000000000100"), --AND tests
    ( "0001", "00000000", "01010101", "00000000", '0', "0000000000000001"), --AND tests
52 ( "0001", "00000000", "10101010", "00000000", '0', "0000000000000001"), --AND tests
    ( "0001", "11111111", "01010101", "01010101", '0', "0000000000000000"), --AND tests
    - 10 ns
54 ( "0001", "11111111", "10101010", "10101010", '0', "0000000000000100"), --AND tests
    ( "0001", "10000011", "10110010", "10000010", '0', "0000000000000100"), --AND tests
56 ( "0001", "00000011", "00110010", "00000010", '0', "0000000000000000"), --AND tests
    - 14 ns
58 ( "0011", "00000000", "00000000", "00000000", '0', "0000000000000001"), --OR tests
    ( "0011", "00000001", "00000001", "00000001", '0', "0000000000000000"), --OR tests
60 ( "0011", "00000000", "00000001", "00000001", '0', "0000000000000000"), --OR tests
    ( "0011", "10101010", "10101010", "10101010", '0', "0000000000000100"), --OR tests
62 ( "0011", "01010101", "01010101", "01010101", '0', "0000000000000000"), --OR tests
    ( "0011", "11111111", "00000000", "11111111", '0', "0000000000000100"), --OR tests
```

```

64  ("0011", "11111111", "11111111", "11111111", '0', "000000000000100"), --OR tests
    - 20 ns
    ("0011", "00000000", "01010101", "01010101", '0', "0000000000000000"), --OR tests
66  ("0011", "00000000", "10101010", "10101010", '0', "000000000000100"), --OR tests
    ("0011", "11111111", "01010101", "11111111", '0', "000000000000100"), --OR tests
68  ("0011", "11111111", "10101010", "11111111", '0', "000000000000100"), --OR tests
    ("0011", "10000011", "10110010", "10110011", '0', "000000000000100"), --OR tests
    - 25 ns
70  ("0011", "00000011", "00110010", "00110011", '0', "0000000000000000"), --OR tests

72  ("0101", "00000000", "00000000", "11111111", '0', "000000000000100"), --NOT tests
    - ry should not matter
    ("0101", "00000001", "00000001", "11111110", '0', "000000000000100"), --NOT tests
74  ("0101", "00000000", "00000001", "11111111", '0', "000000000000100"), --NOT tests
    ("0101", "10101010", "10101010", "01010101", '0', "0000000000000000"), --NOT tests
    - 30 ns
76  ("0101", "01010101", "01010101", "10101010", '0', "000000000000100"), --NOT tests
    ("0101", "11111111", "00000000", "00000000", '0', "0000000000000001"), --NOT tests
78  ("0101", "11111111", "11111111", "00000000", '0', "0000000000000001"), --NOT tests
    ("0101", "00000000", "01010101", "11111111", '0', "000000000000100"), --NOT tests
80  ("0101", "00000000", "10101010", "11111111", '0', "000000000000100"), --NOT tests
    - 35 ns
    ("0101", "11111111", "01010101", "00000000", '0', "0000000000000001"), --NOT tests
82  ("0101", "11111111", "10101010", "00000000", '0', "0000000000000001"), --NOT tests
    ("0101", "10000011", "10110010", "01111100", '0', "0000000000000000"), --NOT tests
84  ("0101", "00000011", "00110010", "11111100", '0', "000000000000100"), --NOT tests
    - 39 ns

86  ("0111", "00000000", "00000000", "00000000", '0', "0000000000000001"), --XOR tests
    - 40 ns
    ("0111", "00000001", "00000001", "00000000", '0', "0000000000000001"), --XOR tests
88  ("0111", "00000000", "00000001", "00000001", '0', "0000000000000000"), --XOR tests
    ("0111", "10101010", "10101010", "00000000", '0', "0000000000000001"), --XOR tests
90  ("0111", "01010101", "01010101", "00000000", '0', "0000000000000001"), --XOR tests
    ("0111", "11111111", "00000000", "11111111", '0', "000000000000100"), --XOR tests
    - 45 ns
92  ("0111", "11111111", "11111111", "00000000", '0', "0000000000000001"), --XOR tests
    ("0111", "00000000", "01010101", "01010101", '0', "0000000000000000"), --XOR tests
94  ("0111", "00000000", "10101010", "10101010", '0', "000000000000100"), --XOR tests
    ("0111", "11111111", "01010101", "10101010", '0', "000000000000100"), --XOR tests
96  ("0111", "11111111", "10101010", "01010101", '0', "0000000000000000"), --XOR tests
    - 50 ns
    ("0111", "10000011", "10110010", "00110001", '0', "0000000000000000"), --XOR tests
98  ("0111", "00000011", "00110010", "00110001", '0', "0000000000000000"), --XOR tests
);
100 begin
    -- Check each pattern.
102 for i in patterns'range loop
    -- Set the inputs.
104 Cin <= patterns(i).Cin;
    f <= patterns(i).f;
106 rx <= patterns(i).rx;
    ry <= patterns(i).ry;
108 -- Wait for the results.
    wait for 1 ns;
110 -- Check the outputs.
    assert ro = patterns(i).ro
112 report "bad output register value" severity error;
    assert sr = patterns(i).sr
114 report "bad status register value" severity error;
    assert sr(0) = patterns(i).sr(0)
116 report "*Zero is incorrect" severity error;
    assert sr(1) = patterns(i).sr(1)
118 report "*Carry is incorrect" severity error;
    assert sr(2) = patterns(i).sr(2)
120 report "*Negative is incorrect" severity error;
end loop;
122 assert false report "end of test" severity note;
    -- Wait forever; this will finish the simulation.
124 wait;
end process;
126 end behav;

```


Listing 25: processor/fulladder_tb.vhd

```

1  -- Authors:
   --      Henry Jenkins, Joel Koh
3
   library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;

7  -- A testbench has no ports.
   entity fulladder8_tb is
9      end fulladder8_tb;

11 architecture behav of fulladder8_tb is
   -- Declaration of the component that will be instantiated.
13     component fulladder8
       Port (A      : in    STD_LOGIC_VECTOR( 7 downto 0);
15           B      : in    STD_LOGIC_VECTOR( 7 downto 0);
           Cin      : in    STD_LOGIC;
17           Sum     : out   STD_LOGIC_VECTOR( 7 downto 0);
           Cout     : out   STD_LOGIC
19       );
       end component;
   -- Specifies which entity is bound with the component.
   for fulladder8_0: fulladder8 use entity work.fulladder8;
23     signal A,B,Sum      : STD_LOGIC_VECTOR (7 downto 0);
       signal Cin,Cout    : STD_LOGIC;
25     begin
       -- Component instantiation.
27     fulladder8_0: fulladder8 port map (A => A, B => B, Cin => Cin, Sum => Sum, Cout
           => Cout);

29     -- This process does the real job.
       process
31         type pattern_type is record
           A      : STD_LOGIC_VECTOR( 7 downto 0);
33           B      : STD_LOGIC_VECTOR( 7 downto 0);
           Cin     : STD_LOGIC;
35           Sum    : STD_LOGIC_VECTOR( 7 downto 0);
           Cout    : STD_LOGIC;
37         end record;
       -- The patterns to apply.
39     type pattern_array is array (natural range <>) of pattern_type;
       constant patterns : pattern_array :=
41     -- A      B      Cin    Sum    Cout
       (( "00000000", "00000000", '0', "00000000", '0'), --AND tests - 1ns
43         ("11111111", "11111111", '1', "11111111", '1'), --AND tests
           ("00000000", "00000000", '1', "00000001", '0'), --AND tests
45         ("00000000", "11111111", '0', "11111111", '0'), --AND tests
           ("11111111", "00000000", '0', "11111111", '0'), --AND tests
47         ("11111111", "00000000", '1', "00000000", '1'), --AND tests
           ("10101010", "01010101", '0', "11111111", '0'), --AND tests
49         ("10101010", "01010101", '1', "00000000", '1'), --AND tests
           ("11111111", "11111111", '0', "11111110", '1') --XOR tests
51     );
       begin
53     -- Check each pattern.
       for i in patterns'range loop
55         -- Set the inputs.
           A <= patterns(i).A;
57         B <= patterns(i).B;
           Cin <= patterns(i).Cin;
59         -- Wait for the results.
           wait for 1 ns;
61         -- Check the outputs.
           assert Sum = patterns(i).Sum
63         report "The sum check failed" severity error;
           assert Cout = patterns(i).Cout
65         report "The carry out is wrong" severity error;
       end loop;
       assert false report "end of test" severity note;
       -- Wait forever; this will finish the simulation.
69     wait;
   end process;

```

71 end behav;

Listing 26: processor/spr_tb.vhd

```
-- Authors:
2 --      Henry Jenkins, Joel Koh

4 library ieee;
use ieee.std_logic_1164.all;
6 --use ieee.std_logic_unsigned.all;
--use ieee.std_logic_arith.all;
8
entity spr_TB is          -- entity declaration
10 end spr_TB;

12 architecture TB of spr_TB is

14     component sr
Port (clk      : in    STD_LOGIC;
16         enable : in    STD_LOGIC;          -- Enable write
        reset   : in    STD_LOGIC;          -- Reset the register
18         Ri     : in    STD_LOGIC_VECTOR (15 downto 0); -- The input to the SPR
        Ro      : out   STD_LOGIC_VECTOR (15 downto 0)); -- The output from SPR
20 end component;

22     signal sr_enable : std_logic;
signal sr_reset  : std_logic;
24     signal sr_Ri     : std_logic_vector(15 downto 0);
signal sr_Ro     : std_logic_vector(15 downto 0);
26
    component pc
28     Port (clk      : in    STD_LOGIC;
        enable : in    STD_LOGIC;          -- Enable write
30         reset   : in    STD_LOGIC;          -- Reset the register
        Ri     : in    STD_LOGIC_VECTOR (15 downto 0); -- The input to the SPR
32         Ro      : out   STD_LOGIC_VECTOR (15 downto 0)); -- The output from SPR
    end component;
34
    signal pc_enable : std_logic;
signal pc_reset  : std_logic;
36     signal pc_Ri     : std_logic_vector(15 downto 0);
signal pc_Ro     : std_logic_vector(15 downto 0);
38
40     signal T_clk : std_logic;

42 begin

44     U_sr: sr port map (clk => T_clk, enable => sr_enable, reset => sr_reset, Ri =>
        sr_Ri, Ro => sr_Ro);
    U_pc: pc port map (clk => T_clk, enable => pc_enable, reset => pc_reset, Ri =>
        pc_Ri, Ro => pc_Ro);
46
    -- concurrent process to offer the clk signal
48 process
begin
50     T_clk <= '0';
    wait for 5 ns;
52     T_clk <= '1';
    wait for 5 ns;
54 end process;

56 process

58     variable err_cnt: integer :=0;

60 begin

62     -- Write
    sr_enable <= '1';
64     sr_reset <= '0';
    sr_Ri     <= "0100011001011001";
66     pc_enable <= '1';
```

```

68     pc_reset    <= '0';
    pc_Ri        <= "0101011010110100";
    wait for 20 ns;

70
    -- Read
72     assert (sr_Ro="0100011001011001") report "Read sr #1 failed" severity error;
    assert (pc_Ro="0101011010110100") report "Read pc #1 failed" severity error;
74
    -- Change Ri
76     sr_Ri <= "1001100101110100";
    pc_Ri <= "0001010001110000";
78     wait for 20 ns;
    assert (sr_Ro = "1001100101110100") report "Read sr #2 failed" severity error;
80     assert (pc_Ro = "0001010001110000") report "Read pc #2 failed" severity error;

82     -- Disable sr, pc still enabled
    sr_enable <= '0';
84     sr_Ri <= "0101010101010101";
    pc_Ri <= "1010101010101010";
86     wait for 20 ns;
    assert (sr_Ro = "1001100101110100") report "Wrote to sr while disabled" severity
        error;
88     assert (pc_Ro = "1010101010101010") report "Read pc #3 failed" severity error;

90     -- Enable sr
    sr_enable <= '1';
92     wait for 20 ns;
    assert (sr_Ro = "0101010101010101") report "Read sr #3 failed" severity error;
94
    -- Disable pc, sr still enabled
96     pc_enable <= '0';
    sr_Ri <= "0000000011111111";
98     pc_Ri <= "1111111100000000";
    wait for 20 ns;
100    assert (sr_Ro = "0000000011111111") report "Read sr #4 failed" severity error;
    assert (pc_Ro = "1010101010101010") report "Wrote to pc while disabled" severity
        error;
102
    -- Enable pc
104    pc_enable <= '1';
    wait for 20 ns;
106    assert (pc_Ro = "1111111100000000") report "Read pc #4 failed" severity error;

108
    assert false report "End of test" severity note;
110    wait; -- wait forever to end the test

112 end process;

114 end TB;

116 -----
117 configuration CFG_TB of spr_TB is
118     for TB
119         end for;
120 end CFG_TB;

```

Listing 27: processor/gpr_tb.vhd

```

-- Authors:
2 --     Henry Jenkins, Joel Koh

4 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

6
-- A testbench has no ports.
8 entity gpr_tb is
    end gpr_tb;

10
architecture behav of gpr_tb is
12     -- Declaration of the component that will be instantiated.
    component gpr

```

```

14  Port(clk                : IN std_logic;                -- Clock
        enable             : IN std_logic;                -- Enable input
        (output is always enabled)
16      SelRx, SelRy, SelRi : IN std_logic_vector(2 DOWNT0 0); -- Selecti which
        registers to use
        Ri                 : IN std_logic_vector(7 DOWNT0 0); -- Input
18      Rx, Ry              : OUT std_logic_vector(7 DOWNT0 0)); -- Outputs
    end component;
20  -- Specifies which entity is bound with the component.
    for gpr_0: gpr use entity work.gpr;
22  signal clk, enable      : std_logic;
    signal SelRx, SelRy, SelRi : std_logic_vector(2 DOWNT0 0);
24  signal Ri, Rx, Ry       : std_logic_vector(7 DOWNT0 0);
begin
26  -- Component instantiation.
    gpr_0: gpr port map (clk => clk, enable => enable, SelRx => SelRx, SelRy => SelRy,
        SelRi => SelRi, Ri => Ri, Rx => Rx, Ry => Ry);
28
    -- Does the clock signal
30  process
    begin
32      clk <= '0';
        wait for 5 ns;
34      clk <= '1';
        wait for 5 ns;
36  end process;

38  -- This process does the real job.
    process
    begin
42      -- Write to R0
        SelRi <= "000";
44      Ri <= "00010100";
        enable <= '1';
46      wait for 20 ns;

48      -- Read R0 from Rx
        SelRx <= "000";
50      wait for 20 ns;
        assert (Rx = "00010100") report "Read from Rx failed #1" severity error;
52
        -- Read R0 from Ry
54      SelRy <= "000";
        wait for 20 ns;
56      assert (Ry = "00010100") report "Read from Ry failed #1" severity error;

58      -- Disable write
        enable <= '0';
60      wait for 20 ns;

62      -- Change Ri (should not write as it is disabled)
        Ri <= "00101010";
64      wait for 20 ns;
        assert (Rx = "00010100") report "Wrote to register while disabled #1" severity
            error;
66      assert (Ry = "00010100") report "Wrote to register while disabled #2" severity
            error;

68      -- Enable write
        enable <= '1';
70      wait for 20 ns;
        assert (Rx = "00101010") report "Read from Rx failed #2" severity error;
72      assert (Ry = "00101010") report "Read from Ry failed #2" severity error;

74      -- Write to R2
        SelRi <= "010";
76      Ri <= "01010001";
        wait for 20 ns;

78      -- Read R2 from Rx
80      SelRx <= "010";
        wait for 20 ns;

```

```

82     assert (Rx = "01010001") report "Read from Rx failed #3" severity error;

84     -- Read R2 from Ry
    SelRy <= "010";
86     wait for 20 ns;
    assert (Ry = "01010001") report "Read from Ry failed #3" severity error;

88     -- Read R0 from Rx again (should not have changed from previous results)
90     SelRx <= "000";
    wait for 20 ns;
92     assert (Rx = "00101010") report "Read from Rx failed #4" severity error;

94     -- Read R0 from Ry again (should not have changed from previous results)
    SelRy <= "000";
96     wait for 20 ns;
    assert (Ry = "00101010") report "Read from Ry failed #4" severity error;

98     -- Wait for a long time
100    wait for 1 ms;
    assert (Rx = "00101010") report "Read from Rx failed #5" severity error;
102    assert (Ry = "00101010") report "Read from Ry failed #5" severity error;

104    -- Read R2 after a long time
    SelRx <= "010";
106    SelRy <= "010";
    wait for 1 ms;
108    assert (Rx = "01010001") report "Read from Rx failed #6" severity error;
    assert (Ry = "01010001") report "Read from Ry failed #6" severity error;
110

112    assert false report "End of test" severity note;
    wait; -- wait forever to end the test
114

    end process;
116 end behav;

```

Listing 28: mmu/mmu_tb.vhd

```

1  -- Author:
   --      Wim Looman
3
   library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;

7  library work;
   use work.mmu_main;
9  use work.minimal_uart_core;
   use work.txt_util.all;
11
   entity mmu_tb is
13 end mmu_tb;

15 architecture tb of mmu_tb is
   component mmu_main is
17     port (
       -- instruction bus
19     inst_add  : in  std_logic_vector(11 downto 0); -- Address lines.
       inst_data : out std_logic_vector(15 downto 0); -- Data lines.
21     inst_req  : in  std_logic; -- Pulled low to request bus
       usage;
       inst_ack  : out std_logic; -- Pulled high to inform of
       request completion.
23     -- data bus
       data_add  : in  std_logic_vector(15 downto 0); -- Address lines.
25     data_line : inout std_logic_vector(7 downto 0); -- Data lines.
       data_read : in  std_logic; -- High for a read request,
       low for a write request.
27     data_req  : in  std_logic; -- Pulled low to request bus
       usage;
       data_ack  : inout std_logic; -- Pulled high to inform of
       request completion.
29     -- extras

```

```

31         clk          : in  std_logic;
        receive_pin    : in  std_logic;
        transfer_pin   : out std_logic
33     );
    end component;

35     component minimal_uart_core is
37     port(
        clock : in    std_logic;
39         eoc   : out   std_logic;
        outp   : inout std_logic_vector(7 downto 0) := "ZZZZZZZZ";
41         rxd   : in    std_logic;
        txd    : out   std_logic;
43         eot   : out   std_logic;
        inp    : in    std_logic_vector(7 downto 0);
45         ready : out   std_logic;
        wr     : in    std_logic
47     );
    end component;

49     signal inst_add      : std_logic_vector(11 downto 0);
51     signal inst_data     : std_logic_vector(15 downto 0);
    signal inst_req       : std_logic := '1';
53     signal inst_ack      : std_logic;
    signal data_add       : std_logic_vector(15 downto 0);
55     signal data_line     : std_logic_vector(7 downto 0);
    signal data_read      : std_logic;
57     signal data_req      : std_logic;
    signal data_ack       : std_logic;
59     signal clk           : std_logic;
    signal receive_pin    : std_logic;
61     signal transfer_pin  : std_logic;

63     signal eoc, rxd, txd, eot, ready, wr: std_logic;
    signal outp, inp : std_logic_vector(7 downto 0);
65
    signal current_rcv : std_logic_vector(7 downto 0);
67     signal current_send : std_logic_vector(7 downto 0);
begin
69     m : mmu_main port map (inst_add, inst_data, inst_req, inst_ack, data_add,
        data_line, data_read, data_req, data_ack, clk, receive_pin, transfer_pin);
    muart : minimal_uart_core port map (clk, eoc, outp, rxd, txd, eot, inp, ready, wr);
71
    rxd <= transfer_pin;
73     receive_pin <= txd;

75     clk_gen : process begin
        clk <= '0';
77         wait for 10 ns;
        clk <= '1';
79         wait for 10 ns;
    end process;

81     inst_test : process
83         type pattern_type is record
            inst_add      : std_logic_vector(11 downto 0);
85             rcv_head     : std_logic_vector( 7 downto 0);
            send_head     : std_logic_vector( 7 downto 0);
87             inst_data    : std_logic_vector(15 downto 0);
        end record;
        type pattern_array is array (natural range <>) of pattern_type;
        constant patterns : pattern_array :=
91 --         inst_add      rcv_head      send_head      inst_data
        ((x"52E", x"81", x"83", x"83A7"),
93         (x"96F", x"81", x"83", x"4F5E"),
        (x"8F1", x"81", x"83", x"5937"),
95         (x"65A", x"81", x"83", x"A8F2"));
    begin
97         wr <= '0';
        for i in patterns'range loop
99             wait for 10000 ns;
            inst_add <= patterns(i).inst_add;
101            wait for 20 ns;

```

```

103     inst_req <= '0';

105     wait until eoc'event;
106     assert outp = patterns(i).recv_head
107         report "Bad header expected '" & str(patterns(i).recv_head) & "' recieved '"
108             & str(outp) & "'"
109         severity error;
110     wait until eoc'event;

112     assert false report "passed header" severity note;

114     wait until eoc'event;
115     assert outp = patterns(i).inst_add(7 downto 0)
116         report "Bad address low expected '" & str(patterns(i).inst_add(7 downto 0)) &
117             "' recieved '" & str(outp) & "'"
118         severity error;
119     wait until eoc'event;

121     assert false report "passed address low" severity note;

123     wait until eoc'event;
124     assert outp = "0000" & patterns(i).inst_add(11 downto 8)
125         report "Bad address high expected '" & str(patterns(i).inst_add(11 downto
126             8)) & "' recieved '" & str(outp) & "'"
127         severity error;
128     wait until eoc'event;

130     assert false report "passed address high" severity note;

132     wait for 100 ns;
133     inp <= patterns(i).send_head;
134     wait for 20 ns;
135     wr <= '1';
136     wait for 20 ns;
137     wr <= '0';
138     wait until eot'event;
139     wait until eot'event;

141     wait for 100 ns;
142     inp <= "0000" & patterns(i).inst_add(11 downto 8);
143     wait for 20 ns;
144     wr <= '1';
145     wait for 20 ns;
146     wr <= '0';
147     wait until eot'event;
148     wait until eot'event;

150     wait for 100 ns;
151     inp <= patterns(i).inst_add(7 downto 0);
152     wait for 20 ns;
153     wr <= '1';
154     wait for 20 ns;
155     wr <= '0';
156     wait until eot'event;
157     wait until eot'event;

159     wait for 100 ns;
160     inp <= patterns(i).inst_data(7 downto 0);
161     wait for 20 ns;
162     wr <= '1';
163     wait for 20 ns;
164     wr <= '0';
165     wait until eot'event;
166     wait until eot'event;

168     wait for 100 ns;
169     inp <= patterns(i).inst_data(15 downto 8);
170     wait for 20 ns;
171     wr <= '1';

```

```

        wait for 20 ns;
173    wr <= '0';
        wait until eot'event;
175    wait until eot'event;

177    assert inst_ack = '1'
        report "receipt not acknowledged"
179        severity error;

181    assert inst_data = patterns(i).inst_data
        report "Wrong data recieve expected '" & str(patterns(i).inst_data) & "'
            recieved '" & str(inst_data) & "'"
183        severity error;

185    assert false report "finished transmission" severity note;

187    wait for 20 ns;

189    inst_req <= '1';
        end loop;
191    wait;
        end process;
193 end tb;

```

Listing 29: data_tb.vhd

```

1  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

3
   library work;
5  use work.mmu_main;
   use work.minimal_uart_core;
7  use work.txt_util.all;

9  entity data_tb is
   end data_tb;

11
   architecture tb of data_tb is
13     component mmu_main is
         port (
15         -- instruction bus
            inst_add  : in  std_logic_vector(11 downto 0); -- Address lines.
17         inst_data  : out std_logic_vector(15 downto 0); -- Data lines.
            inst_req  : in  std_logic;                      -- Pulled low to request bus
                usage.
19         inst_ack   : out std_logic;                      -- Pulled high to inform of
                request completion.
            -- data bus
21         data_add   : in  std_logic_vector(15 downto 0); -- Address lines.
            data_line : inout std_logic_vector(7 downto 0); -- Data lines.
23         data_read  : in  std_logic;                      -- High for a read request,
                low for a write request.
            data_req  : in  std_logic;                      -- Pulled low to request bus
                usage.
25         data_ack   : inout std_logic;                    -- Pulled high to inform of
                request completion.
            -- extras
27         clk        : in  std_logic;
            receive_pin : in  std_logic;
29         transfer_pin : out std_logic
        );
31     end component;

33     component IO is
         PORT(
35         -- data bus --
            data_add   : IN      std_logic_vector(15 DOWNT0 0); -- address lines --
37         data_data   : INOUT    std_logic_vector(7 DOWNT0 0); -- data lines --
            data_read  : INOUT    std_logic;                    -- pulled high for read, low
                for write --
39         data_req    : INOUT    std_logic;                    -- pulled low to request bus
                usage --

```



```

        data_ack      : INOUT    std_logic;                                -- pulled high to inform
        request completion --
41    -- io --
        clk           : IN       std_logic;
43    sw1             : IN       std_logic;
        sw2           : IN       std_logic
45    );
end component;

47    component minimal_uart_core is
49    port(
        clock : in      std_logic;
51    eoc      : out     std_logic;
        outp   : inout   std_logic_vector(7 downto 0) := "ZZZZZZZZ";
53    rxd      : in      std_logic;
        txd    : out     std_logic;
55    eot      : out     std_logic;
        inp    : in      std_logic_vector(7 downto 0);
57    ready    : out     std_logic;
        wr     : in      std_logic
59    );
end component;

61
63    signal inst_add      : std_logic_vector(11 downto 0);
        signal inst_data  : std_logic_vector(15 downto 0);
        signal inst_req   : std_logic := '1';
65    signal inst_ack      : std_logic;
        signal data_add    : std_logic_vector(15 downto 0);
67    signal data_line     : std_logic_vector(7 downto 0);
        signal data_read   : std_logic;
69    signal data_req      : std_logic;
        signal data_ack     : std_logic;
71    signal clk           : std_logic;
        signal receive_pin  : std_logic;
73    signal transfer_pin  : std_logic;
        signal sw1, sw2 : std_logic;
75
        signal eoc, rxd, txd, eot, ready, wr : std_logic;
77    signal outp, inp : std_logic_vector(7 downto 0);
begin
79    m : mmu_main port map (inst_add, inst_data, inst_req, inst_ack, data_add,
        data_line, data_read, data_req, data_ack, clk, receive_pin, transfer_pin);
        i : IO port map (data_add, data_line, data_read, data_req, data_ack, clk,
            sw1, sw2);
81    muart : minimal_uart_core port map (clk, eoc, outp, rxd, txd, eot, inp, ready, wr);

83    rxd <= transfer_pin;
        receive_pin <= txd;
85
        clk_gen : process begin
87            clk <= '0';
                wait for 10 ns;
89            clk <= '1';
                wait for 10 ns;
91        end process;

93    data_test : process
        type pattern_type is record
95        data_add      : std_logic_vector(15 downto 0);
            recv_head   : std_logic_vector( 7 downto 0);
97        send_head     : std_logic_vector( 7 downto 0);
            data_data    : std_logic_vector( 7 downto 0);
99        switch_data   : std_logic_vector( 1 downto 0);
            rw           : std_logic;
101    end record;
        type pattern_array is array (natural range <>) of pattern_type;
103    constant patterns : pattern_array :=
-- data_add, recv_head, send_head, data_data, switch_data, rw
105    ((x"0581", x"80", x"00", x"A7", "00", '1' ),
        (x"0273", x"00", x"00", x"5E", "00", '0' ));
107    begin
        wr <= '0';
109    data_req <= '1';

```

```

111     for i in patterns'range loop
112         wait for 10000 ns;
113         data_add <= patterns(i).data_add;
114         data_read <= patterns(i).rw;
115         wait for 20 ns;
116         if patterns(i).rw = '0' then
117             data_line <= patterns(1).data_data;
118         else
119             data_line <= (others => 'Z');
120         end if;
121         wait for 20 ns;
122         data_req <= '0';
123
124     if patterns(i).data_add(0) = '1' then
125         wait until eoc'event;
126         assert outp = patterns(i).recv_head
127             report "Bad header expected '" & str(patterns(i).recv_head) & "' recieved
128                 '" & str(outp) & '"
129             severity error;
130         wait until eoc'event;
131
132         assert false report "passed header" severity note;
133
134         wait until eoc'event;
135         assert outp = patterns(i).data_add(8 downto 1)
136             report "Bad address low expected '" & str(patterns(i).data_add(7 downto
137                 0)) & "' recieved '" & str(outp) & '"
138             severity error;
139         wait until eoc'event;
140
141         assert false report "passed address low" severity note;
142
143         wait until eoc'event;
144         assert outp = "0" & patterns(i).data_add(15 downto 9)
145             report "Bad address high expected '" & str(patterns(i).data_add(11 downto
146                 8)) & "' recieved '" & str(outp) & '"
147             severity error;
148         wait until eoc'event;
149
150         assert false report "passed address high" severity note;
151         if patterns(i).rw = '0' then
152             wait until eoc'event;
153             assert outp = patterns(i).data_data
154                 report "Bad data expected '" & str(patterns(i).data_data) & "' recieved
155                     '" & str(outp) & '"
156             severity error;
157             wait until eoc'event;
158
159             assert false report "passed data" severity note;
160         else
161             wait for 100 ns;
162             inp <= patterns(i).send_head;
163             wait for 20 ns;
164             wr <= '1';
165             wait for 20 ns;
166             wr <= '0';
167             wait until eot'event;
168             wait until eot'event;
169
170             wait for 100 ns;
171             inp <= patterns(i).data_add(8 downto 1);
172             wait for 20 ns;
173             wr <= '1';
174             wait for 20 ns;
175             wr <= '0';
176             wait until eot'event;
177             wait until eot'event;
178
179             wait for 100 ns;
180             inp <= "0" & patterns(i).data_add(15 downto 9);
181             wait for 20 ns;

```

```

179         wr <= '1';
180         wait for 20 ns;
181         wr <= '0';
182         wait until eot'event;
183         wait until eot'event;

185
186         wait for 100 ns;
187         inp <= patterns(i).data_data;
188         wait for 20 ns;
189         wr <= '1';
190         wait for 20 ns;
191         wr <= '0';
192         wait until eot'event;
193         wait until eot'event;
194     end if;
195 else
196
197 end if;

199 assert data_ack = '1'
200     report "receipt not acknowledged"
201     severity error;

203 if patterns(i).rw = '1' then
204     assert data_line = patterns(i).data_data
205         report "Wrong data recieve expected '" & str(patterns(i).data_data) & "'
206             recieved '" & str(data_line) & "'"
207             severity error;
208 end if;

209 assert false report "finished transmission" severity note;

211 wait for 20 ns;

213 data_req <= '1';
214 end loop;
215 wait;
216 end process;
217 end tb;

```

Tools

Listing 30: assembler.rb

```
1 #!/usr/bin/env ruby

3 # Author:
4 #     Wim Looman
5 # Copyright:
6 #     Copyright (c) 2010 Wim Looman
7 # License:
8 #     GNU General Public License (see http://www.gnu.org/licenses/gpl-3.0.txt)
9
10 def assert(error=nil)
11   raise (error || "Assertion Failed!") unless yield
12 end
13
14 # For 8-bit twos complement
15 def twos_complement(num)
16   return 256 + num
17 end
18
19
20 def logical_operands(chunks)
21   y = chunks[1][1..1].to_i
22   assert(chunks[1] + " is not a valid register") {y >= 0 && y < 8}
23   x = chunks[2][1..1].to_i
24   assert(chunks[2] + " is not a valid register") {x >= 0 && x < 8}
25   return (y << 5) + x
26 end
27
28
29 def immediate(chunk, symbols=nil, move_from=nil)
30   v = chunk.to_i
31   if v == 0 && chunk != "0" && symbols != nil
32     assert(chunk + " is not a valid symbol") {symbols.include?(chunk)}
33     move_to = symbols[chunk]
34     diff = move_to - move_from
35     if diff < 1
36       diff = twos_complement(diff)
37     end
38     return diff
39   else
40     assert(chunk + " is not a valid immediate") {v >= -127 && v < 128}
41     if v < 0
42       v = twos_complement(v)
43     end
44     return v
45   end
46 end
47
48
49 def register(chunk, num_registers)
50   x = chunk[1..1].to_i
51   assert(chunk + " is not a valid register") {x >= 0 && x < num_registers}
52   return x
53 end
54
55
56 def auto(chunk)
57   if chunk[-1..-1] == "+"
58     return 0x08
59   elsif chunk[-1..-1] == "-"
60     return 0x10
61   else
62     return 0x00
63   end
64 end
65
66
67 def convert(lines)
68   table = first_pass(lines)
```

```

69     return second_pass(lines, table)
70 end
71
72
73 def first_pass(lines)
74     instruction = 0
75     symbols = {}
76     lines.each do |line|
77         chunks = line.sub(" ", " ").split
78         case chunks[0]
79             when "LDI", "LD", "STI", "ST", "MV", "AND", "OR", "NOT", "XOR", "ADD", "ADC",
              "SUB", "SBB", "NEG", "CMP", "BEQ", "BNE", "BLT", "BGT", "BC", "BNC", "RJMP",
              "JMP"
              instruction += 1
81
              when "label:"
83                 symbols[chunks[1]] = instruction
84             end
85         end
86     return symbols
87 end
88
89 def second_pass(lines, symbols)
90     line_no = 0
91     output = []
92     lines.each do |line|
93         label = line.sub(" ", " ").split[0]
94         case label
95             when "LDI", "LD", "STI", "ST", "MV", "AND", "OR", "NOT", "XOR", "ADD", "ADC",
              "SUB", "SBB", "NEG", "CMP", "BEQ", "BNE", "BLT", "BGT", "BC", "BNC", "RJMP",
              "JMP"
97                 line_no += 1
98                 output.push(convert_line(line, symbols, line_no))
99             end
100         end
101     return output.flatten
102 end
103
104
105 def convert_line(line, symbols, line_no)
106     chunks = line.sub(" ", " ").split#.partition(";")[0].split
107
108     case chunks[0]
109         when "LDI"
110             instruction = 0x21
111             x = register(chunks[1], 4)
112             v = immediate(chunks[2])
113             operands = (v << 2) + x
114
115         when "LD"
116             instruction = 0x01 + auto(chunks[2])
117             x = register(chunks[1], 8)
118             y = register(chunks[2], 3)
119             operands = (y << 5) + x
120
121         when "STI"
122             instruction = 0x25
123             y = register(chunks[1], 3)
124             v = immediate(chunks[2])
125             operands = (v << 2) + y
126
127         when "ST"
128             instruction = 0x05 + auto(chunks[1])
129             y = register(chunks[1], 3)
130             x = register(chunks[2], 8)
131             operands = (y << 5) + x
132
133         when "MV"
134             instruction = 0x04
135             if chunks[1][0] == 'r'[0] && chunks[2][0] == 'r'[0]
136                 y = register(chunks[1], 8)
137                 x = register(chunks[2], 8)

```

```

139     operands = (y << 5) + x
140 elif chunks[1][0] == 'a'[0]
141     y = register(chunks[1], 3)
142     x = register(chunks[2], 8)
143     n = chunks[1][-1] == 'H' ? 1 : 0
144     operands = (1 << 9) + (n << 8) + (y << 5) + x
145 elif chunks[2][0] == 'a'[0]
146     y = register(chunks[1], 8)
147     x = register(chunks[2], 3)
148     n = chunks[2][-1] == 'H' ? 1 : 0
149     operands = (1 << 4) + (n << 3) + (y << 5) + x
150 else
151     # explode
152 end
153
154 when "AND"
155     instruction = 0x02
156     operands = logical_operands(chunks)
157
158 when "OR"
159     instruction = 0x06
160     operands = logical_operands(chunks)
161
162 when "NOT"
163     instruction = 0x0A
164     operands = logical_operands(chunks)
165
166 when "XOR"
167     instruction = 0x0E
168     operands = logical_operands(chunks)
169
170 when "ADD"
171     instruction = 0x12
172     operands = logical_operands(chunks)
173
174 when "ADC"
175     instruction = 0x16
176     operands = logical_operands(chunks)
177
178 when "SUB"
179     instruction = 0x1A
180     operands = logical_operands(chunks)
181
182 when "SBB"
183     instruction = 0x1E
184     operands = logical_operands(chunks)
185
186 when "NEG"
187     instruction = 0x08
188     operands = logical_operands(chunks)
189
190 when "CMP"
191     instruction = 0x0C
192     operands = logical_operands(chunks)
193
194 when "BEQ"
195     instruction = 0x23
196     v = immediate(chunks[1], symbols, line_no)
197     operands = (v << 2)
198
199 when "BNE"
200     instruction = 0x27
201     v = immediate(chunks[1], symbols, line_no)
202     operands = (v << 2)
203
204 when "BLT"
205     instruction = 0x2B
206     v = immediate(chunks[1], symbols, line_no)
207     operands = (v << 2)
208
209 when "BGT"
210     instruction = 0x2F
211     v = immediate(chunks[1], symbols, line_no)

```

```

211     operands = (v << 2)

213     when "BC"
214         instruction = 0x33
215         v = immediate(chunks[1], symbols, line_no)
216         operands = (v << 2)

217     when "BNC"
218         instruction = 0x37
219         v = immediate(chunks[1], symbols, line_no)
220         operands = (v << 2)

221     when "RJMPP"
222         instruction = 0x3B
223         v = immediate(chunks[1], symbols, line_no)
224         operands = (v << 2)

225     when "JMP"
226         instruction = 0x2F
227         y = register(chunks[1], 3)
228         operands = (y << 5)
229     end
230     opcode = (instruction << 10) + operands
231     return [(opcode >> 8), (opcode & 0xFF)]
232 end

233 if __FILE__ == $0
234     if !(1..2).include?(ARGV.length) || !File.exist?(ARGV[0])
235         p "Usage: ruby #{__FILE__} <input_file> [<output_file>]"
236         exit
237     end

238     input = IO.readlines(ARGV[0])

239     output = convert(input)
240     if ARGV.length == 2:
241         File.open(ARGV[1], "wb") do |file|
242             output.each do |char|
243                 file.putc(char)
244             end
245         end
246     else
247         output.each do |char|
248             $stdout.putc(char)
249         end
250     end
251 end
end

```

Listing 31: memory.rb

```

#!/usr/bin/env ruby
2
# Author:
4 #     Wim Looman
# Copyright:
6 #     Copyright (c) 2010 Wim Looman
# License:
8 #     GNU General Public License (see http://www.gnu.org/licenses/gpl-3.0.txt)

10 require 'rubygems'
11 require 'serialport'
12
13 def serve(program, data_file, sp)
14     while 1
15         header = sp.getc
16         diagnostic_mode = (header >> 2) & 0x03
17         instruction = header & 0x01 == 0x01
18         address = sp.getc + (sp.getc << 8)

20         case (header >> 7) & 0x01 # read/write bit
21             when 0x01             # read

```

```

22     header = 0x82
23     header += 0x01 if instruction
24     sp.putc(header)
25     instruction ? sp.write(program[address]) :
26         sp.write(data_file[address])
27     p "Sending data for #{instruction ? "Instruction" : "Data"} bus, address:" +
28         "#{address}, data: #{instruction ? program[address] : data_file[address]}"
29     when 0x00 # write, doesn't support writing to instruction memory
30         data = sp.getc
31         data_file[address] = data
32     p "Writing data, address: " + address + ", data: " + data_file[address]
33     end
34 end
35 end
36
37 if __FILE__ == $0
38     if ARGV.size < 3
39         STDERR.print "Usage: ruby #{$0} <device> <baud_rate> <program_file>
40             [<data_file>]\n"
41         exit
42     end
43
44     device = ARGV[0]
45     baud_rate = ARGV[1].to_i
46
47     program = Array.new(2**12, 0x00)
48     i = 0
49     File.open(ARGV[2], 'rb') do |input|
50         input.each_byte do |byte|
51             program[i] = byte
52             i += 1
53         end
54     end
55
56     data = Array.new(2**15, 0x00)
57     File.open(ARGV[3], 'rb') do |input|
58         input.each_byte do |byte|
59             data += byte
60         end
61     end if ARGV.size > 3
62
63     sp = SerialPort.new(device, baud_rate, 8, 1, SerialPort::NONE)
64
65     serve(program, data, sp)
66 end

```
